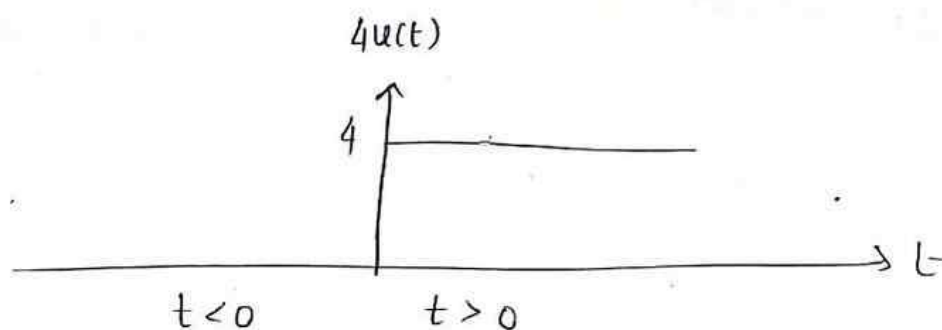


<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)

Answer

①




↓
It gives initial condition.

⇒ Initial current

$$i_L(0^-) = 0 \text{ Amps}$$

t > 0

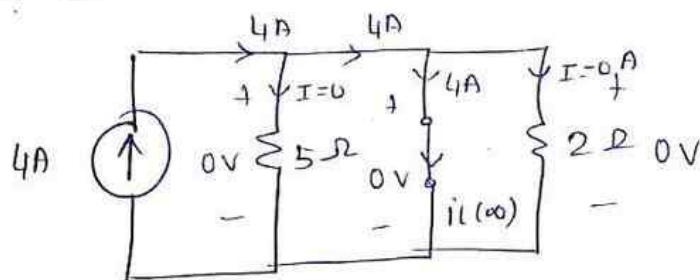⊗ Current source is connected, therefore inductor is short circuited.




$$\therefore i_L(\infty) = 4 \text{ A}$$

⊗ It gives steady state condition.

Time constant

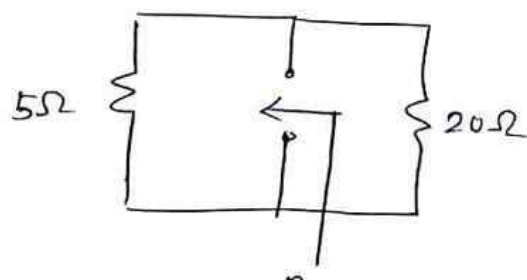⇒ while finding R_{eq} across inductor, the current source become open circuited



KOD

Both 5Ω & 20Ω resistors are parallel.

$$R_{eq} = (5 \parallel 20) \\ = \frac{5 \times 20}{25}$$

$$R_{eq} = 4\Omega$$

Time constant

$$\tau = L/R_{eq} \\ = 8/4$$

$$\boxed{\tau = 2 \text{ seconds}}$$

Inductor current

$$i_L(t) = i_L(\infty) + [i_L(0^-) - i_L(\infty)] e^{-t/\tau}$$

$$i_L(t) = 4 + [0 - 4] e^{-t/2} \text{ Amps}$$

$$\boxed{i_L(t) = 4 - 4e^{-t/2} \text{ Amps}}$$

voltage across inductor = voltage across 20Ω

$$v_L(t) = v(t)$$

$$v(t) = L \frac{di_L(t)}{dt}$$

$$v(t) = 8 \frac{d}{dt} [4 - 4e^{-t/2}]$$

$$v(t) = 8 [-4 \times (-1/2) e^{-t/2}]$$

$$\boxed{v(t) = 16e^{-t/2} \text{ volts}} \quad t > 0$$

Likes: 0

Dislikes: 0
