

Brac University

Semester: Summer 2023

Course Code: CSE250

Circuits And Electronics

Section: 23



Faculty: PRM

Set

B

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
 ✓ At the end of the exam, the **answer script** must be returned to the invigilator.
 ✓ **All questions** are compulsory. Marks allotted for each question are mentioned beside each question.
 ✓ Symbols have their usual meanings.

■ Question 1 of 2 [CO3] [5 marks]

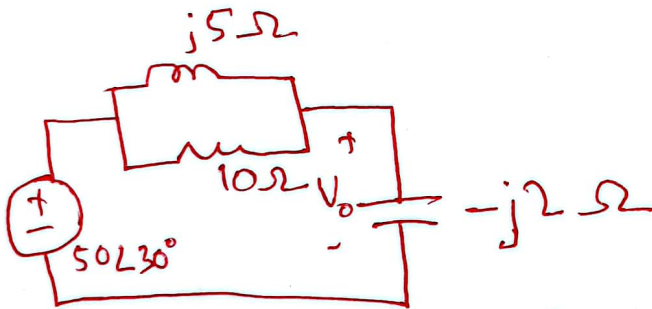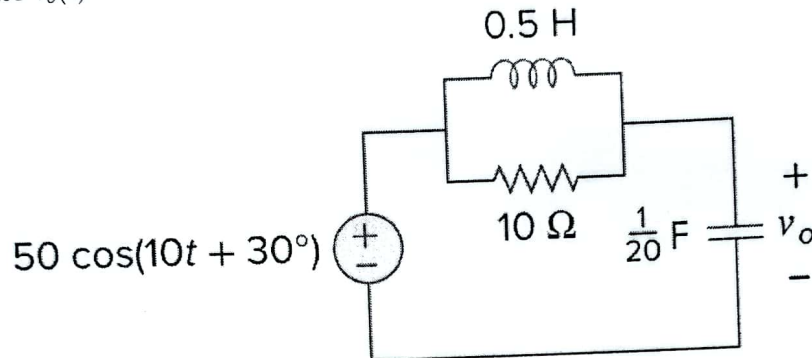Calculate $v_o(t)$ 



$$Z_p = \left(\frac{1}{j5} + \frac{1}{10} \right)^{-1} = 2 + j4$$

$$\therefore V_o = \frac{-j2}{Z_p - j2} \times 50 \angle 30^\circ = 35.36 \angle -105^\circ \text{ V}$$

$$\therefore v_o(t) = 35.36 \cos(10t - 105^\circ) \text{ V}$$


■ Question 2 of 2 [CO3] [15 marks]

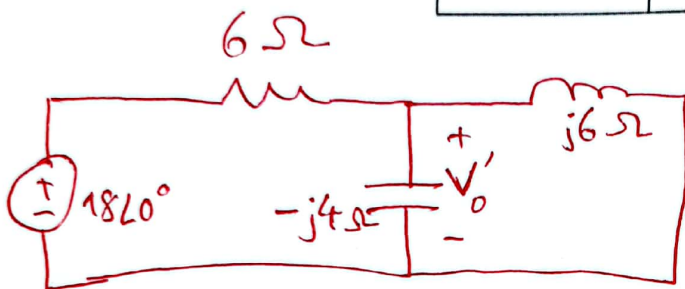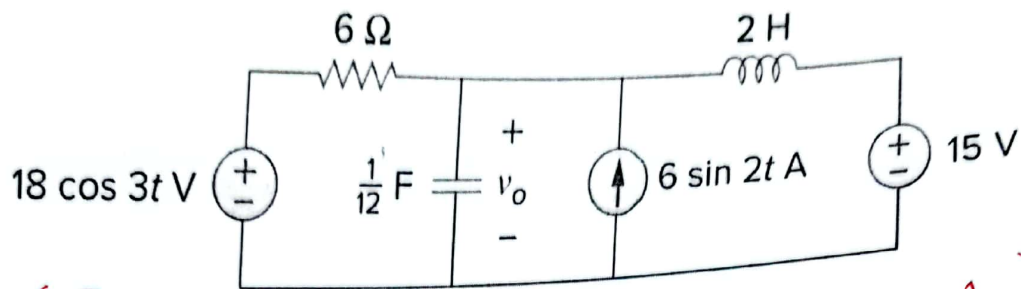Calculate $v_o(t)$ using Superposition Principle.




$$Z_p = \left(\frac{1}{j6} + \frac{1}{-j4} \right)^{-1} = -j12 \Omega$$
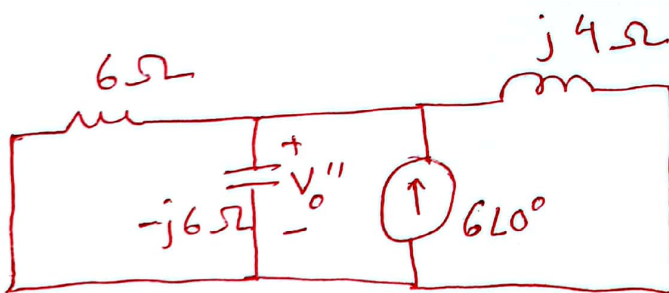
$$\therefore V_o' = \frac{-j12}{6 - j12} \times 18 \angle 0^\circ = 16.1 \angle -26.57^\circ \text{ V}$$



$$Z_p = \left(\frac{1}{6} - \frac{1}{j6} + \frac{1}{j4} \right)^{-1} = 4.8 + j2.4$$
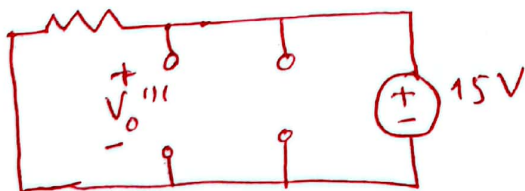
$$\therefore V_o'' = 6 \angle 0^\circ \times Z_p = 32.2 \angle 26.57^\circ \text{ V}$$



$$V_o''' = 15 \text{ V}$$

$$\therefore v_o(t) = 16.1 \cos(3t - 26.57^\circ) + 32.2 \sin(2t + 26.57^\circ) + 15 \text{ V}$$