

Brac University

Semester: Summer 2023

Course Code: CSE250

Circuits And Electronics

Section: 23

Faculty: PRM



Set

A

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, the **answer script** must be returned to the invigilator.
- ✓ All questions are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Symbols have their usual meanings.

■ Question 1 of 2 [CO1] [10 marks]

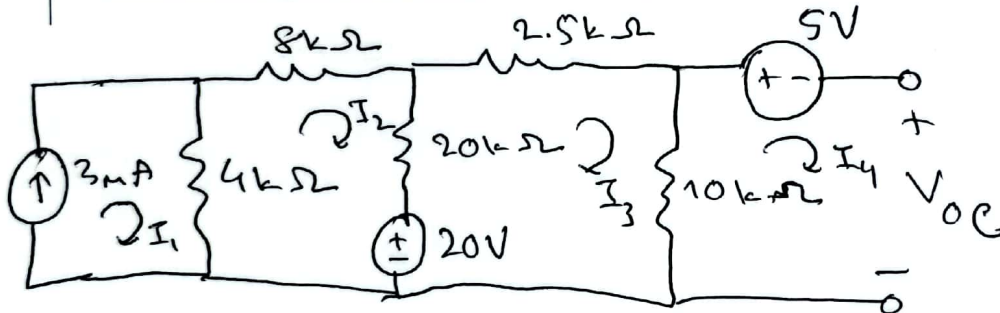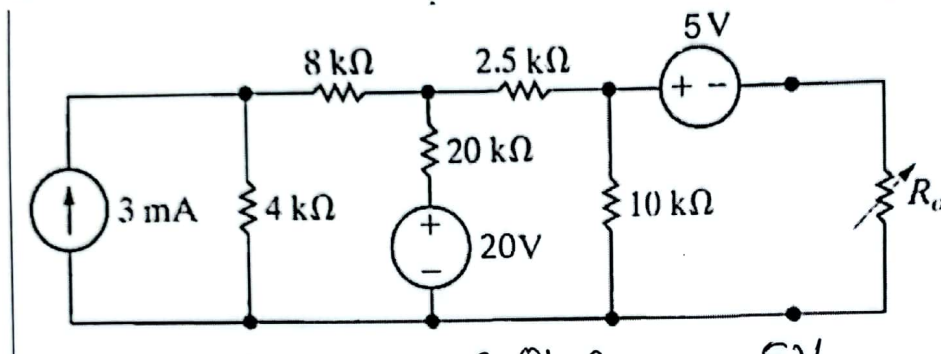Determine the value of V_{th} , I_N and R_{th} of the following circuit considering R_o as the load. Then **draw** either the Thevenin or Norton equivalent circuit.



$$I_1 = 3\text{mA}, I_4 = 0\text{mA (as open circuit)}$$

Applying KVL to mesh 2,

$$4(I_2 - I_1) + 8I_2 + 20(I_2 - I_3) + 20 = 0$$

$$\text{or, } 32I_2 - 20I_3 = -8 \quad \text{--- (1)}$$

Applying KVL to mesh 3,

$$-20 + 20(I_3 - I_2) + 2.5I_3 + 10I_3 = 0$$

$$\text{or, } -20I_2 + 32.5I_3 = 20 \quad \text{--- (2)}$$

Solving equations (i) and (ii) we get,


$$I_2 = 0.22 \text{ mA}, I_3 = 0.75 \text{ mA}$$

Applying KVL to mesh 4,


$$-10I_3 + 5 + V_{oc} = 0$$

$$\text{or, } V_{oc} = 10I_3 - 5 = 2.5 \text{ V} = V_{th}$$

For $R_{th} \Rightarrow$

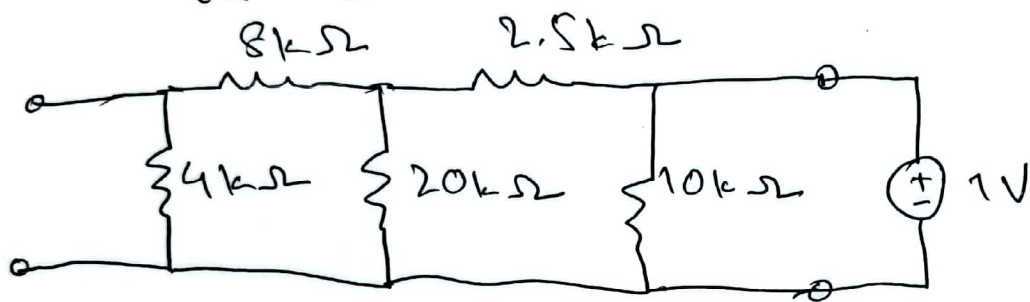

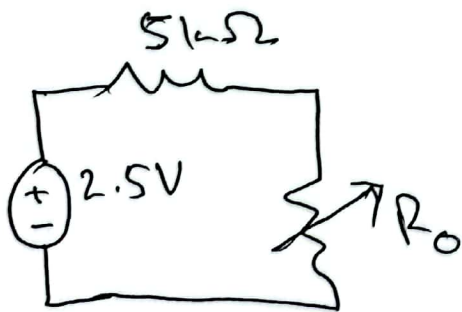
$$\therefore R_{th} = 10 \parallel [2.5 + 20 \parallel (8 + 4)]$$
$$= 5 \text{ k}\Omega$$



$$I_N = \frac{V_{th}}{R_{th}} = 0.5 \text{ mA}$$

■ Question 2 of 2 [CO2] [10 marks]

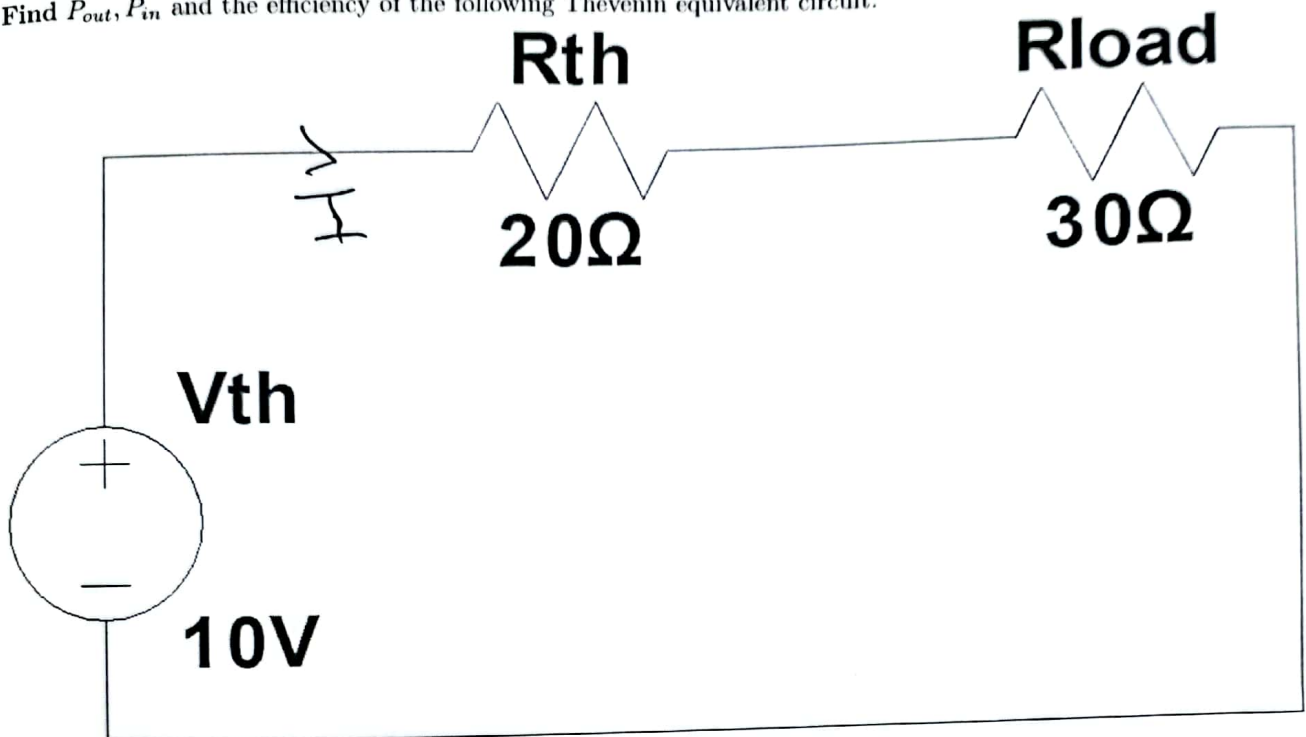Find P_{out} , P_{in} and the efficiency of the following Thevenin equivalent circuit.



$$R_{eq} = 20 + 30 = 50\Omega$$

$$I = \frac{V_{th}}{R_{eq}} = \frac{10}{50} = 0.2A$$

$$P_{out} = I^2 R_{load} = 0.2^2 \times 30 = 1.2W$$

$$P_{in} = V_{th} I = 10 \times 0.2 = 2W$$

$$\begin{aligned} \text{Efficiency, } \eta &= \frac{P_{out}}{P_{in}} \times 100\% \\ &= \frac{1.2}{2} \times 100\% \\ &= 60\% \end{aligned}$$

ID:

Name:

Brac University

Semester: Summer 2023

Course Code: CSE250

Circuits And Electronics

Section: 23

Faculty: PRM

Set

B

Inspiring Excellence


Assessment: Quiz-3

Full Marks: 20

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, the answer script must be returned to the invigilator.
- ✓ All questions are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Symbols have their usual meanings.

■ Question 1 of 2 [CO2] [10 marks]

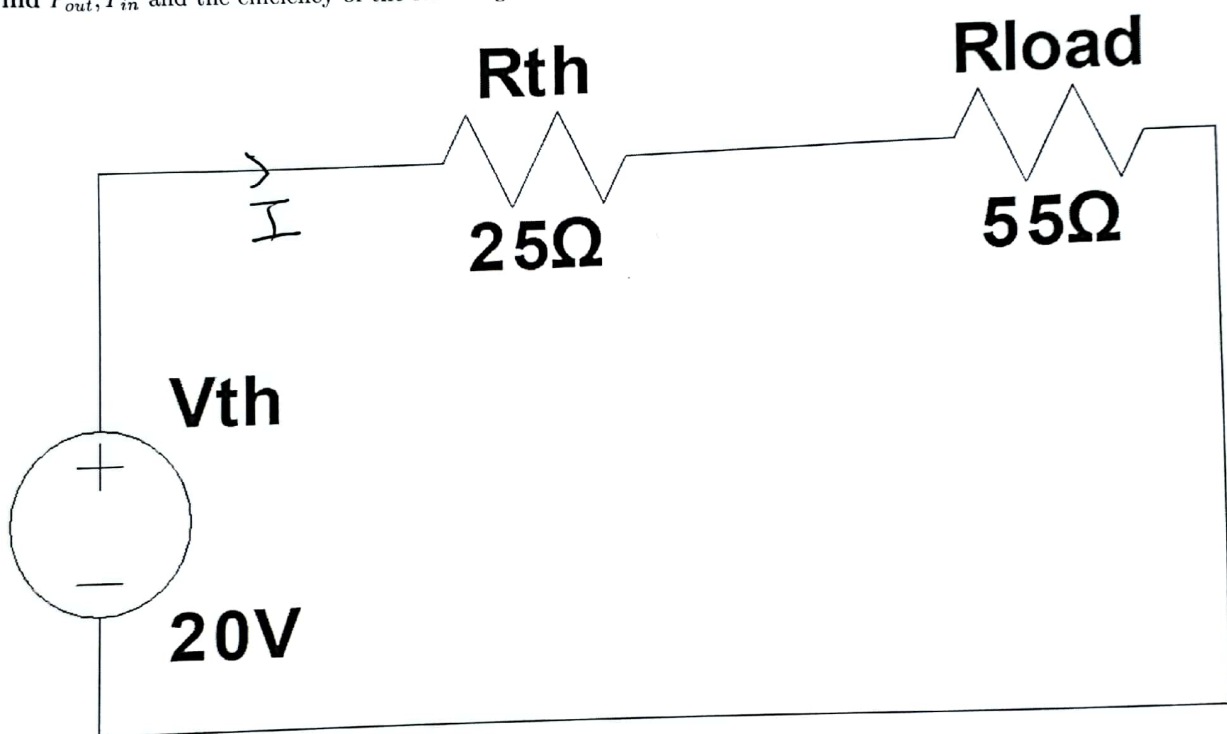Find P_{out} , P_{in} and the efficiency of the following Thevenin equivalent circuit.



$$R_{eq} = 25 + 55 = 80\Omega$$

$$I = \frac{V_{th}}{R_{eq}} = \frac{20}{80} = 0.25A$$


$$\therefore P_{out} = I^2 R_{load} = 0.25^2 \times 55 = 3.4375W$$

$$P_{in} = V_{th} I = 20 \times 0.25 = 5W$$

$$\therefore \text{Efficiency, } \eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{3.4375}{5} \times 100\% = 68.75\%$$

■ Question 2 of 2 [CO1] [10 marks]

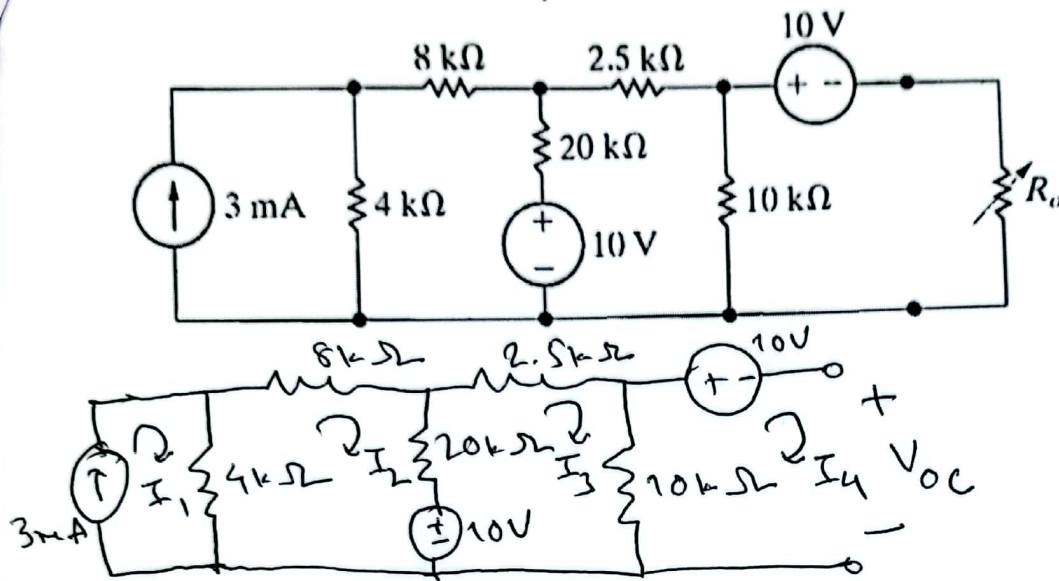Determine the value of V_{th} , I_N and R_{th} of the following circuit considering R_o as the load. Then draw either the Thevenin or Norton equivalent circuit.



$$I_1 = 3\text{mA}, I_4 = 0\text{mA (as open circuit)}$$

Applying KVL on mesh-2,

$$4(I_2 - I_1) + 8I_2 + 20(I_2 - I_3) + 10 = 0$$

$$\therefore, 32I_2 - 20I_3 = 2 \quad \text{--- (1)}$$

Applying KVL on mesh-3,

$$-10 + 20(I_3 - I_2) + 2.5I_3 + 10I_3 = 0$$

$$\therefore, -20I_2 + 32.5I_3 = 10$$

$$\therefore, -20I_2 + 32.5I_3 = 10 \quad \text{--- (11)}$$

Solving equations (1) and (11) we get,


$$I_2 = 0.47\text{mA}, I_3 = 0.56\text{mA}$$

Applying KVL to loop 4,

$$-10I_3 + 10 + V_{oc} = 0$$

$$\text{or, } V_{oc} = 10I_3 - 10 = -4.4V = V_{th}$$

For $R_{th} \Rightarrow$

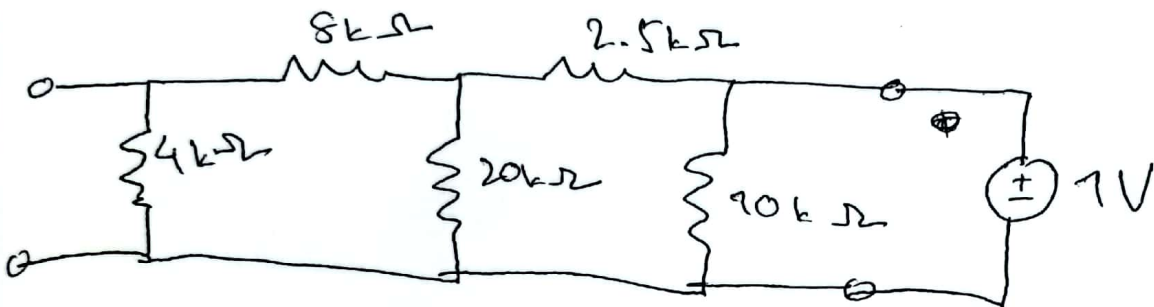

$$\therefore R_{th} = 10 \parallel [2.5 + 20 \parallel (8 + 4)]$$

$$= 5k\Omega$$

$$\therefore I_N = \frac{V_{th}}{R_{th}} = -0.88mA$$

