

Value of x, y for Questions 1, 2

$y \rightarrow$ Last two digits of your ID


$x \rightarrow$ 3rd and 4th last digits
of your ID

For example, if your ID is


21201354, then $x = 13$ and

$y = 54$
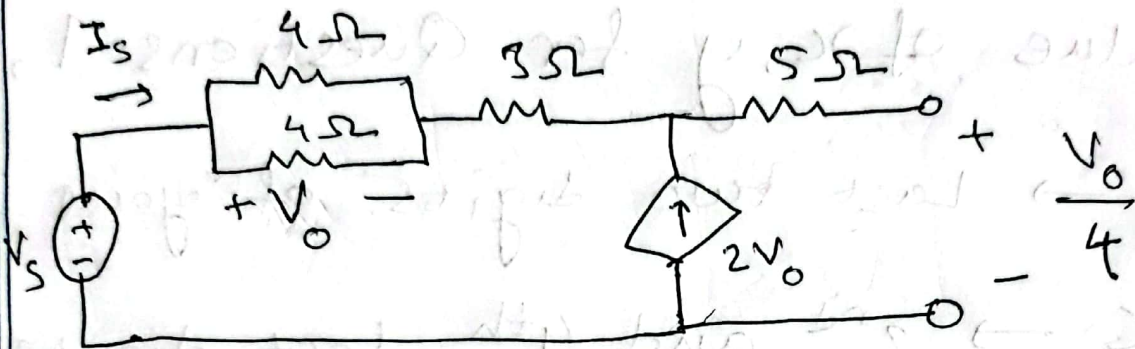
$$1) q_s = x [5 - e^{-6yt} + \sin(4xt)]$$




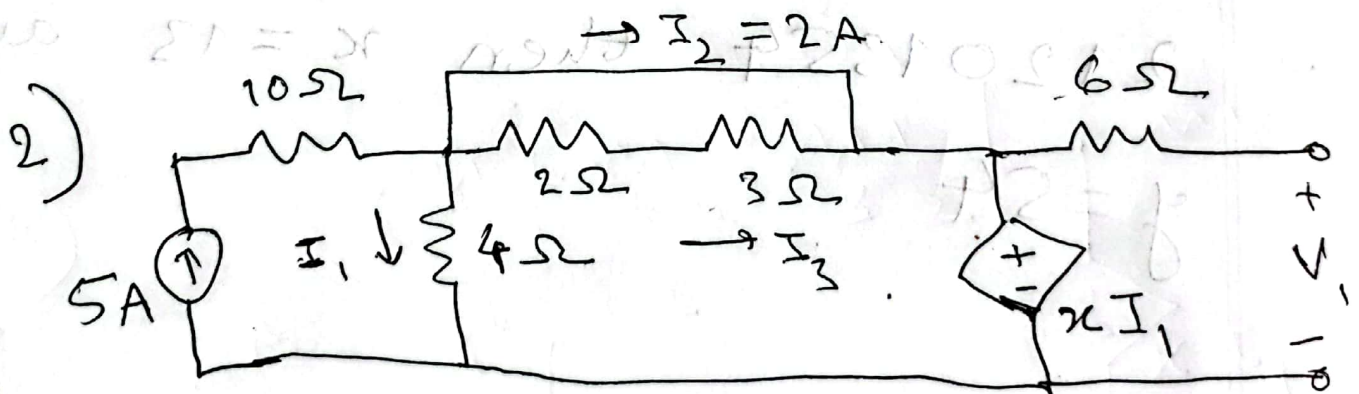Find V_o , I_s and the power supplied/absorbed by the dependent source for $t = 0.1s$.




Find I_1 , I_3 , V_1 and the number of nodes. (label the nodes)

3)

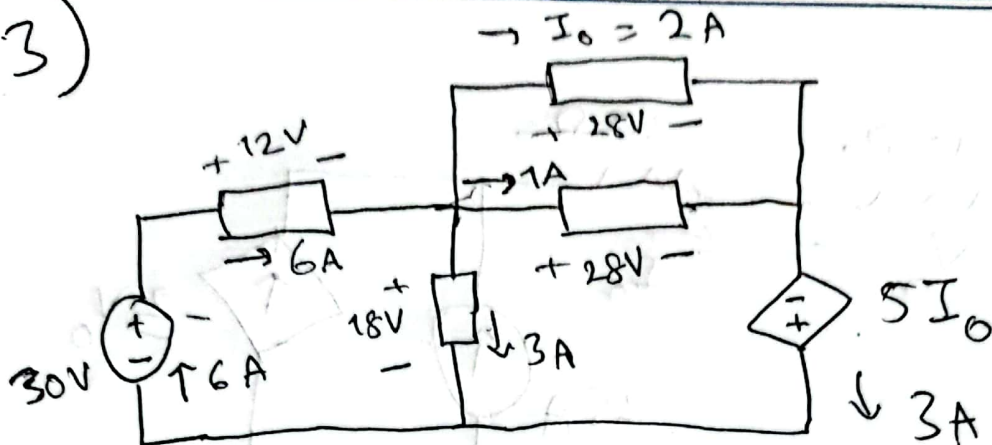


Find ~~the~~ the power supplied/absorbed by each element in the circuit.

4)

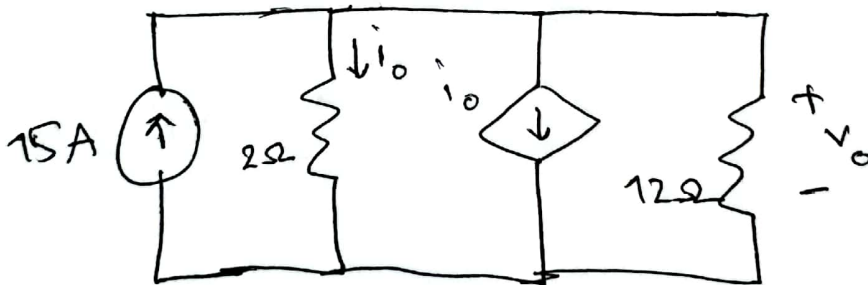

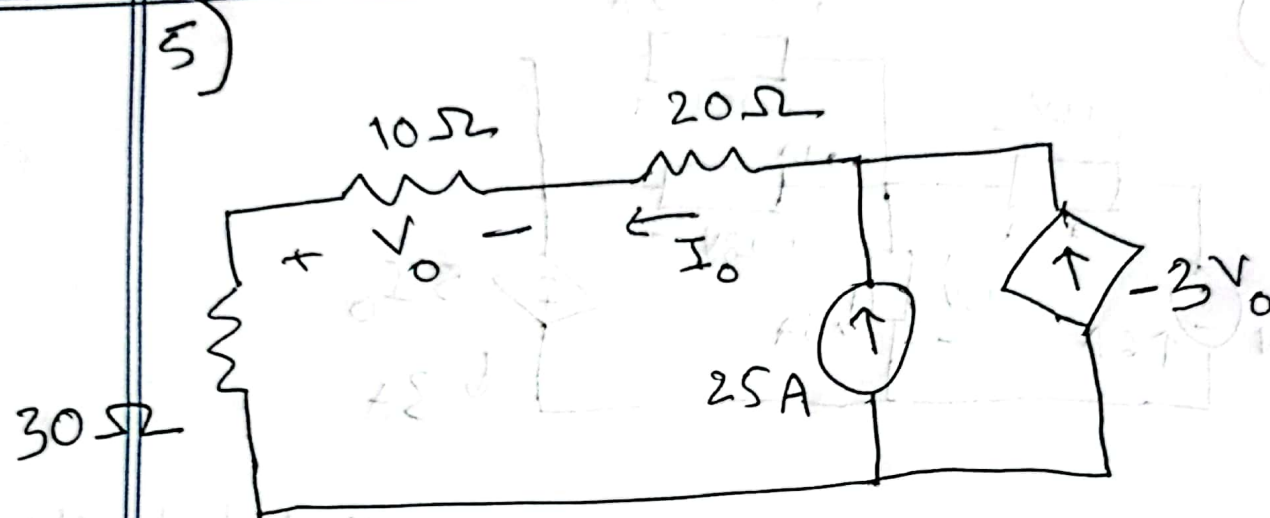Find v_0 , i_0 and the power supplied/absorbed by the dependent source.



Find V_o , I_o and power supplied / absorbed by the dependent source