

<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)

Answer

Step 1 > To determine

Calculate the output voltage across the capacitor v_o in the given circuit of Figure 7.112.

Step 2 > Answer

The output voltage across the capacitor v_o is $[20 - 15e^{-14.286t}]u(t)$ V.

Step 3 > Explanation

Given data:

Refer to Figure 7.112 in the textbook.

The value of capacitance (C) is $3\mu\text{F}$.

The source voltage v_s is $30u(t)$ V.

The initial capacitor voltage $v_o(0)$ is 5 V.

Formula used:

Write the general expression to find the complete voltage response for an RC circuit.

$$v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-\frac{t}{\tau}} \quad (1)$$

Here,

τ is the time constant for the RC circuit,

$v_o(0)$ is the initial capacitor voltage, and

$v_o(\infty)$ is the final capacitor voltage.

Write the expression to find the time constant for an RC circuit.

$$\tau = R_{\text{Th}}C \quad (2)$$

Here,

R_{Th} is the Thevenin resistance, and

C is the capacitance of the capacitor.

Write the general expression for the unit step function.

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases} \quad (3)$$

Calculation:

The initial capacitor voltage,

$$v_o(0) = 5V \quad (4)$$

Apply the unit step function in equation (3) to equation (4).

$$\begin{aligned} v_o(0) &= (5V)u(t) \\ &= 5u(t)V \end{aligned}$$

The given Figure 7.112 is redrawn as shown in Figure 1.

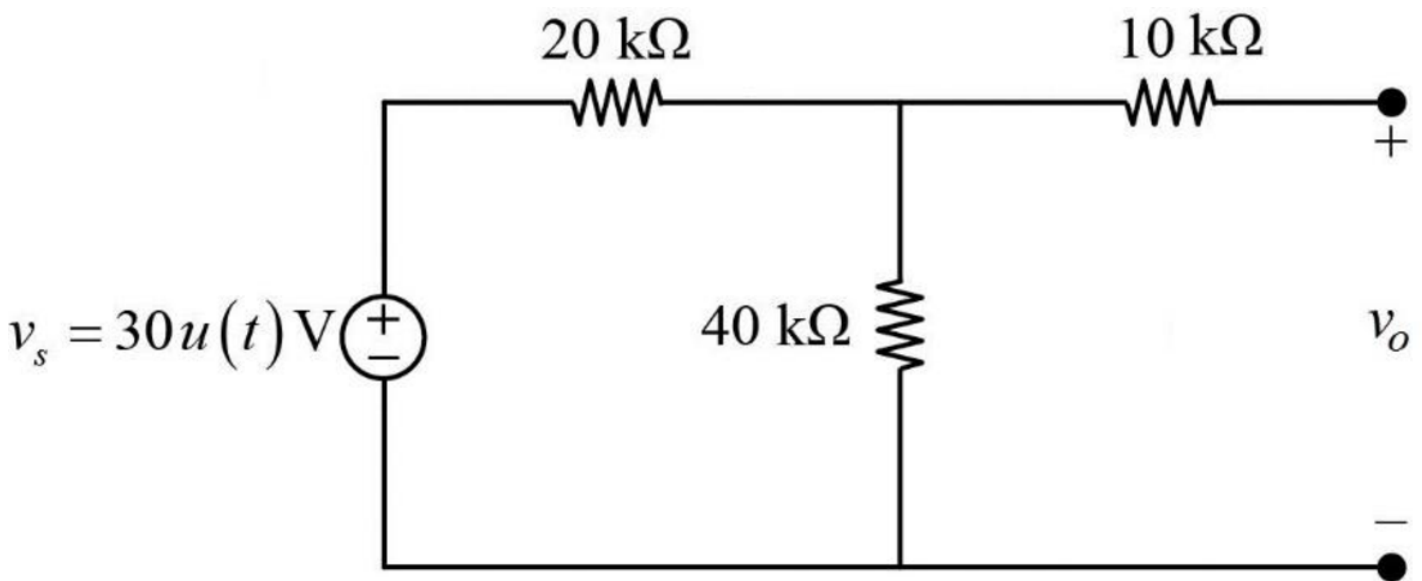


Figure 1

From Figure 1, the final capacitor voltage $v_o(\infty)$ calculated by using voltage division rule.

$$\begin{aligned} v_o(\infty) &= (30u(t)V) \left(\frac{40\text{k}\Omega}{40\text{k}\Omega + 20\text{k}\Omega} \right) \\ &= (30u(t)V) \left(\frac{4}{6} \right) \\ &= 20u(t)V \end{aligned}$$

Figure 2 shows the Thevenin resistance R_{Th} at the capacitor terminal.

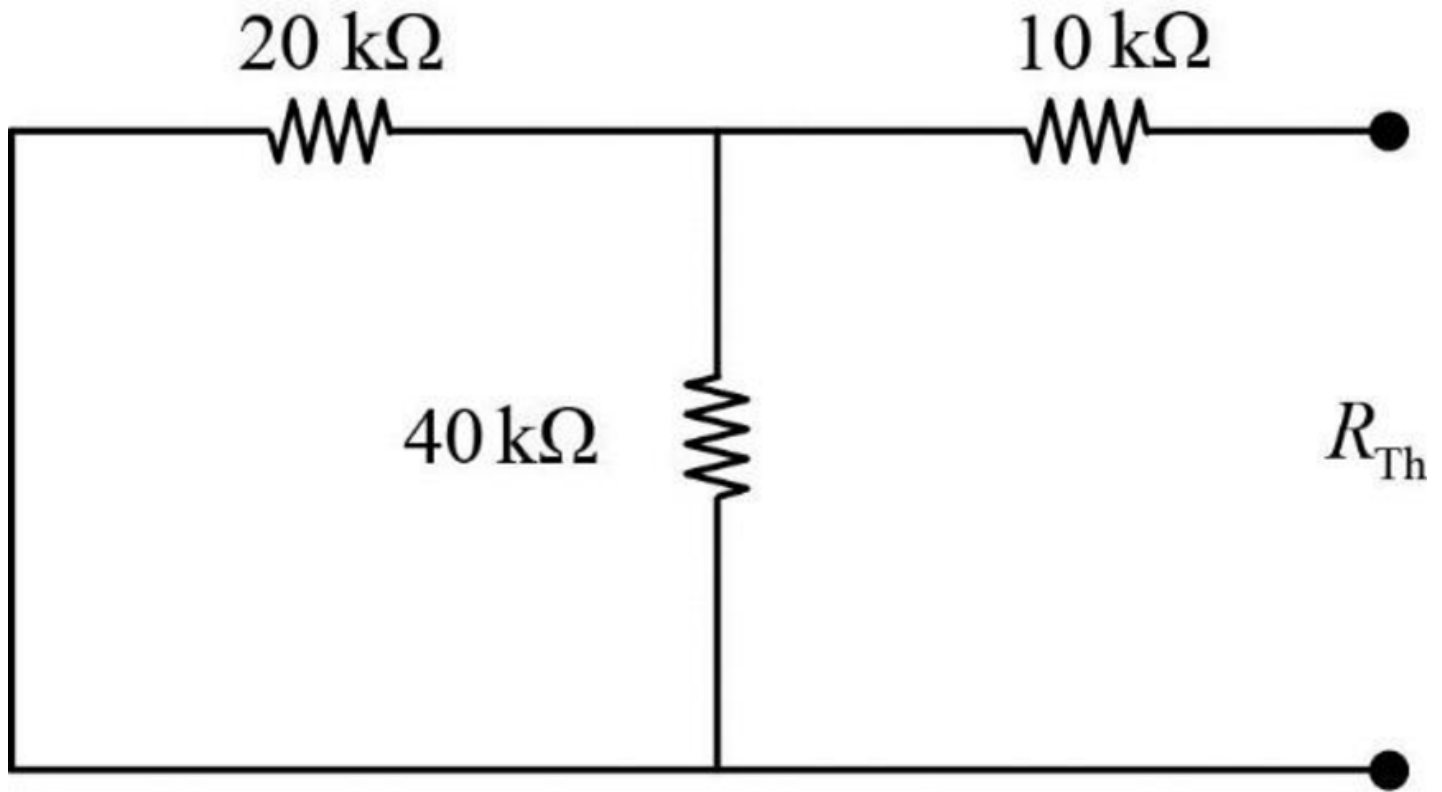


Figure 2

The Thevenin resistance R_{Th} at the capacitor terminal calculated as follows.

$$\begin{aligned}
 R_{Th} &= (20\text{k}\Omega || 40\text{k}\Omega) + 10\text{k}\Omega \\
 &= \left(\frac{20\text{k}\Omega \times 40\text{k}\Omega}{20\text{k}\Omega + 40\text{k}\Omega} \right) + 10\text{k}\Omega \\
 &= \left(\frac{20 \times 40}{60} \right) \text{k}\Omega + 10\text{k}\Omega \\
 &= \left(\frac{40}{3} \right) \text{k}\Omega + 10\text{k}\Omega
 \end{aligned}$$

Simplify the equation as follows,

$$R_{Th} = \frac{70}{3} \text{k}\Omega$$

Substitute $\frac{70}{3} \text{k}\Omega$ for R_{Th} and $3\mu\text{F}$ for C in equation (2) to find the time constant τ .

$$\tau = \left(\frac{70}{3} \text{k}\Omega \right) (3\mu\text{F})$$

$$\tau = \left(\frac{70}{3} \times 10^3 \Omega \right) (3 \times 10^{-6} \text{F}) \left\{ \because 1\text{k} = 10^3, 1\mu = 10^{-6} \right\} \quad (5)$$

Substitute the units $\frac{\text{V}}{\text{A}}$ for Ω and $\frac{\text{A}\cdot\text{s}}{\text{V}}$ for F in equation (5) to find the time constant τ in seconds.

$$\begin{aligned}\tau &= \left(\frac{70}{3} \times 10^3 \frac{\text{V}}{\text{A}}\right) \left(3 \times 10^{-6} \frac{\text{A}\cdot\text{s}}{\text{V}}\right) \\ &= 0.07\text{s}\end{aligned}$$

Substitute $5u(t)\text{V}$ for $v_o(0)$, $20u(t)\text{V}$ for $v_o(\infty)$, and 0.07s for τ in equation (1) to find the output voltage across the capacitor v_o in volts.

$$\begin{aligned}v_o &= 20u(t)\text{V} + [5u(t)\text{V} - 20u(t)\text{V}]e^{-\frac{t}{0.07\text{s}}} \{\because v_o = v_o(t)\} \\ &= 20u(t)\text{V} - 15u(t)\text{V}e^{-14.286t}\end{aligned}$$

$$v_o = [20 - 15e^{-14.286t}]u(t)\text{V}$$

Conclusion:

Thus, the output voltage across the capacitor v_o is $[20 - 15e^{-14.286t}]u(t)\text{V}$.