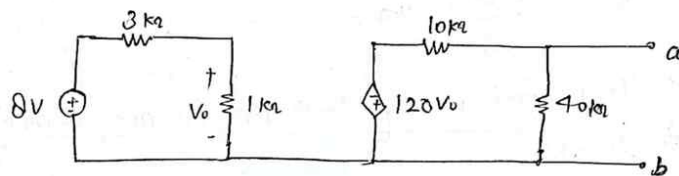


<< Search more Solutions!

**Found Errors in Solution? >> [Report here!](#)**

**Answer**


Soln: The ckt given to us can be represented as:



We need to find  $R_L$  across terminal a-b for maximum power transfer. for  $P_{max}$

$$R_L = R_{th}$$

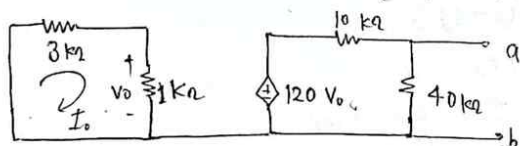⇒ To find the  $R_{th}$  across terminal (a-b) we have to short ckt all the independent source (i.e.  $8V = 0V$ ), then ckt become



On Apply KVL in left side loop, we get


$$3I_0 + 4I_0 = 0$$

$$7I_0 = 0$$

$$I_0 = 0$$

$$V_0 = 1 \times I_0 = 0$$

$$V_0 = 0$$

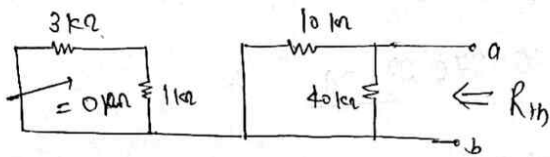


$$R_{th} = (10k\Omega) \parallel (40k\Omega)$$

$$R_{th} = \frac{10 \times 40}{50}$$


$$R_{th} = \frac{400}{50} = 8k\Omega$$
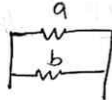
$$\left\{ R_{ab} = \frac{a \cdot b}{a+b} \right\}$$



Hence, the required value of load resistance across terminal a-b is  $8k\Omega$ .

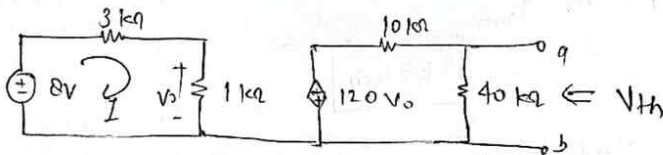⇒ Now, we have to find  $V_{th} = ?$  across terminal a-b as:-



Apply KVL in left side loop, we get

$$-8 + (3+1)I_0 = 0$$

$$4I_0 = 8$$

$$I_0 = \frac{8}{4} = 2mA$$

$$V_0 = 1k\Omega \times 2mA = 2V$$

$$V_{th} = \frac{40}{40+10} \times (120 \times 2) = \frac{40}{50} \times 240 = 192V$$

The maximum power is given by:

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

$$P_{max} = \frac{(192)^2}{4 \times 8} = 1152 \text{ watt}$$

$$\therefore P_{max} = 1152 \text{ watt}$$