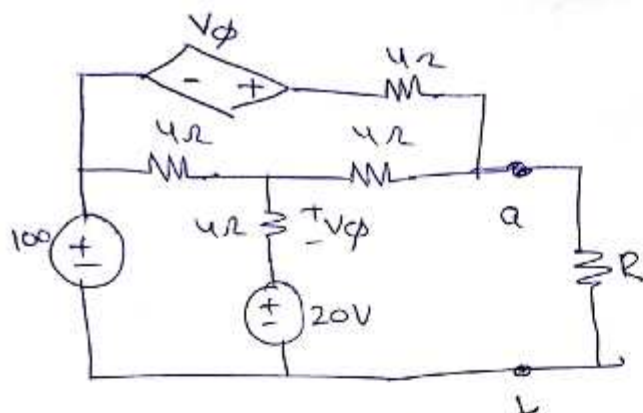


<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)

Answer




we have to calculate the value of R as Thevenin's resistance

where Thevenin's Resistance $R_{th} = \frac{V_{oc}}{I_{sc}}$

V_{oc} - open circuit voltage

I_{sc} - short circuit current

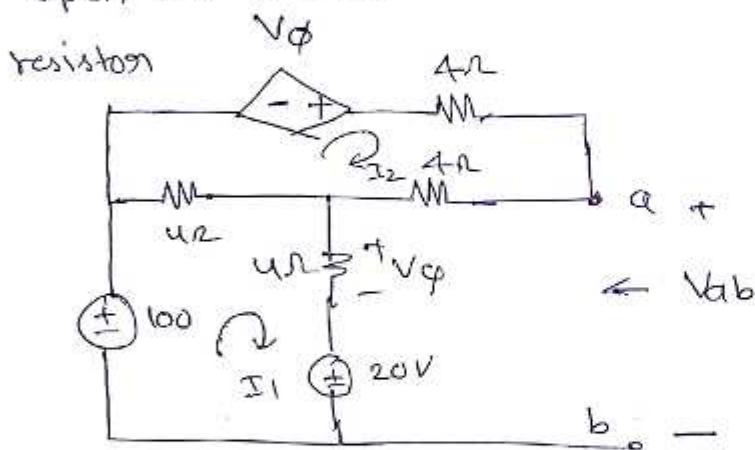open the resistor and calculate the voltage across the resistor



Apply mesh analysis

$$-100 + 4(I_1 - I_2) + 4I_1 + 20 = 0$$

$$8I_1 - 4I_2 = 80$$

$$2I_1 - I_2 = 20 \rightarrow \textcircled{1}$$

and loop 2

$$4(I_2 - I_1) - V_\phi + 4I_2 + 4I_2 = 0$$

$$\text{and } V_\phi = 4I_1$$

$$\Rightarrow 4I_2 - 4I_1 - 4I_1 + 4I_2 + 4I_2 = 0$$

$$I_2 - I_1 - I_1 + I_2 + I_2 = 0$$

by solving equ $\textcircled{1}$

8

$\textcircled{2}$

we get

$$I_1 = 15A$$

$$I_2 = 10A$$

$$3I_2 - 2I_1 = 0 \rightarrow (2)$$

$$-V_{ab} + 4\Omega I_2 + 4I_1 + 20 = 0$$


$$V_{ab} = 4I_2 + 4I_1 + 20$$

$$= 4 \times 10 + 4 \times 15 + 20 = 40 + 60 + 20$$

$$= 160 + 120 + 20 = 120V$$

$$\boxed{V_{ab} = 120V}$$

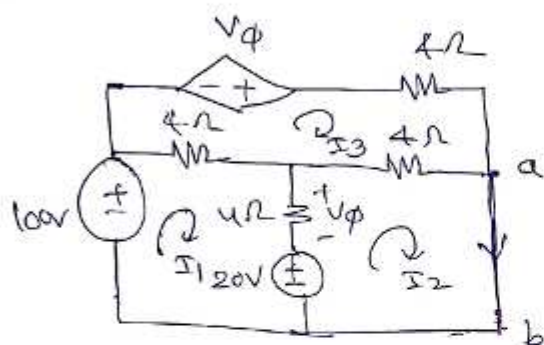make short circuit between ab and calculate I_{sc} (short circuit current)



Apply mesh analysis

$$-100 + 4(I_1 - I_3) + 4(I_1 - I_2) + 20 = 0$$

$$-100 + 8I_1 - 4I_2 - 4I_3 + 20 = 0$$

$$8I_1 - 4I_2 - 4I_3 = 80$$

$$2I_1 - I_2 - I_3 = 20 \rightarrow \textcircled{1}$$

$$-20 + 4(I_2 - I_1) + 4(I_2 - I_3) = 0$$

$$-5 + I_2 - I_1 + I_2 - I_3 = 0 \Rightarrow 2I_2 - I_1 - I_3 = 5 \rightarrow \textcircled{2}$$

$$4(I_3 - I_1) - V_\phi + 4I_3 + 4(I_3 - I_2) = 0$$

$$\text{where } V_\phi = (I_1 - I_2)4$$

$$4(I_3 - I_1) - 4(I_1 - I_2) + 4I_3 + 4(I_3 - I_2) = 0$$

$$I_3 - I_1 - I_1 + I_2 + I_3 + I_3 - I_2 = 0$$

$$3I_3 - 2I_1 = 0 \rightarrow \textcircled{3}$$

by solving equations $\textcircled{1}$, $\textcircled{2}$ & $\textcircled{3}$ we get

$$I_1 = 45, I_2 = 40, I_3 = 30$$


Here short circuit current $I_{sc} = 40A = I_2$

$$\text{So } R_{th} = \frac{300}{40} = 7.5\Omega$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{120V}{40A} = 3\Omega$$

$$I_{sc} = 40A$$

The equivalent circuit becomes

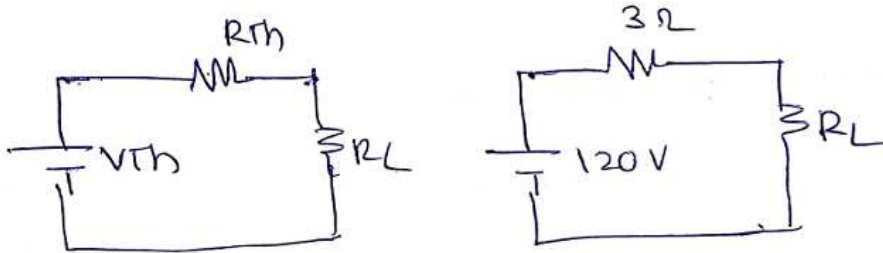

maximum power transfer when $R_L = R_{th} = 3\Omega$

$$\begin{aligned} \textcircled{b} \text{ maximum power transfer} &= \frac{(V_{th})^2}{4 \times R_{th}} = P_{max} \\ &= \frac{(120)^2}{4 \times 3} \end{aligned}$$

$$P_{max} = 1200W$$

$$\boxed{P_{max} = 1.2kW}$$

Likes: 3

Dislikes: 0