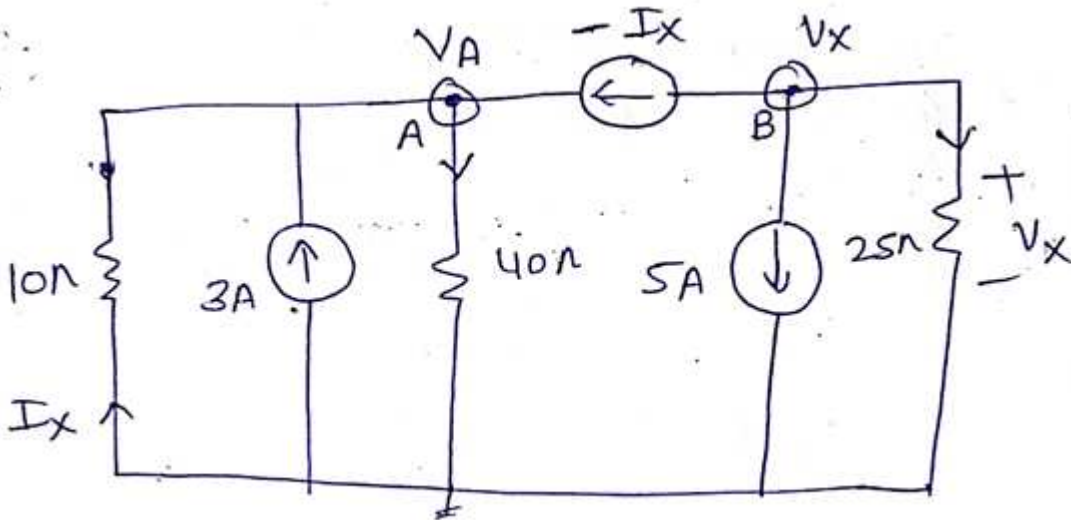


Found Errors in Solution? >> [Report here!](#)

Answer

(a)

The labelled circuit diagram is:



The KCL equation at node 'A':

$$\frac{V_A}{10} + \frac{V_A}{40} = 3 - I_x$$

$$4V_A + V_A = 120 - 40I_x$$

$$5V_A + 40I_x = 120 \dots\dots (1)$$

The voltage across 10-ohm resistor:

$$V_A = -10I_x \dots (2)$$

Put the value of equation (2) into (1)

$$5(-10I_x) + 40I_x = 120$$

$$-10I_x = 120$$

$$I_X = -12 \text{ A}$$

The KCL equation at node 'B':

$$-I_X + 5 + \frac{V_X}{25} = 0$$


$$V_X = 25 \times (I_X - 5)$$

$$V_X = 25 \times (-12 - 5) = -425 \text{ V}$$

$$\mathbf{V_X = -425 \text{ V}}$$

(B)

The labelled circuit diagram is:

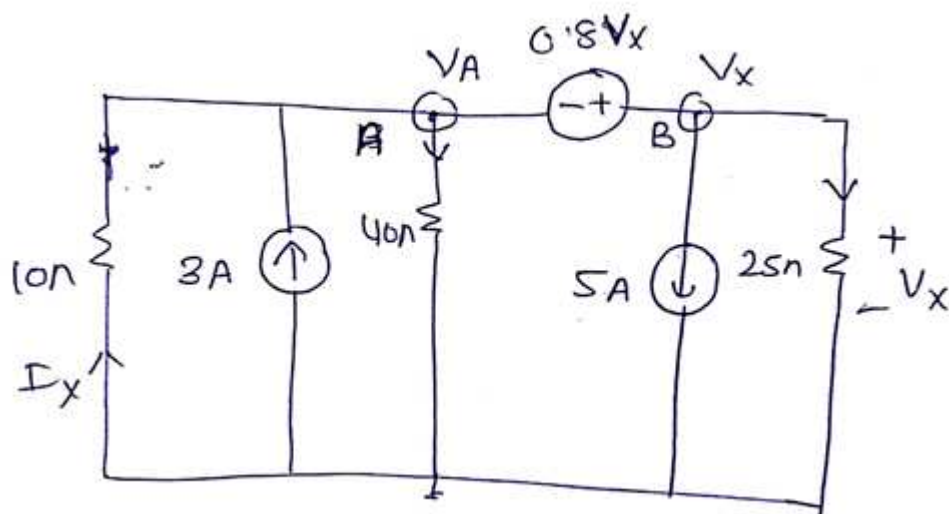

The KCL equation at node 'A':

$$\frac{V_A}{10} + \frac{V_A}{40} + \frac{V_X}{25} + 5 = 3$$

$$20V_A + 5V_A + 8V_X + 1000 = 600$$

$$25V_A + 8V_X = -400 \dots\dots (3)$$

The voltage difference between node 'A' and node 'B':

$$V_A + 0.8V_X = V_X$$

$$V_A = 0.2V_X \dots\dots\dots (4)$$

Put the equation (4) into equation (3)


$$25(0.2V_X) + 8V_X = -400$$

$$V_X = \frac{-400}{13} = -30.77 \text{ V}$$

$$\mathbf{V_X = -30.77 \text{ V}}$$

(c)

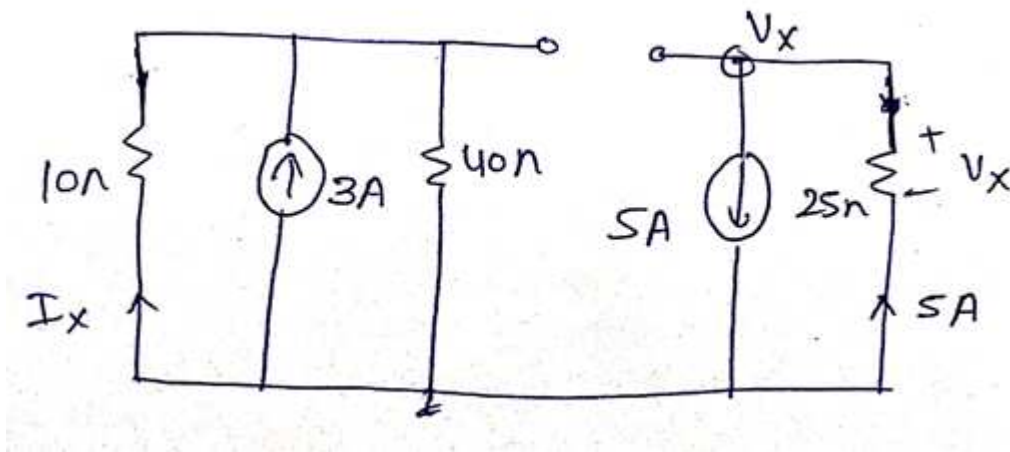When the element A is open circuit then The labelled circuit diagram is:




The voltage V_X is:

$$V_X = 25 \times (-5) = -125 \text{ V}$$

$$\mathbf{V_X = -125 \text{ V}}$$

(d)

The labelled circuit diagram is:

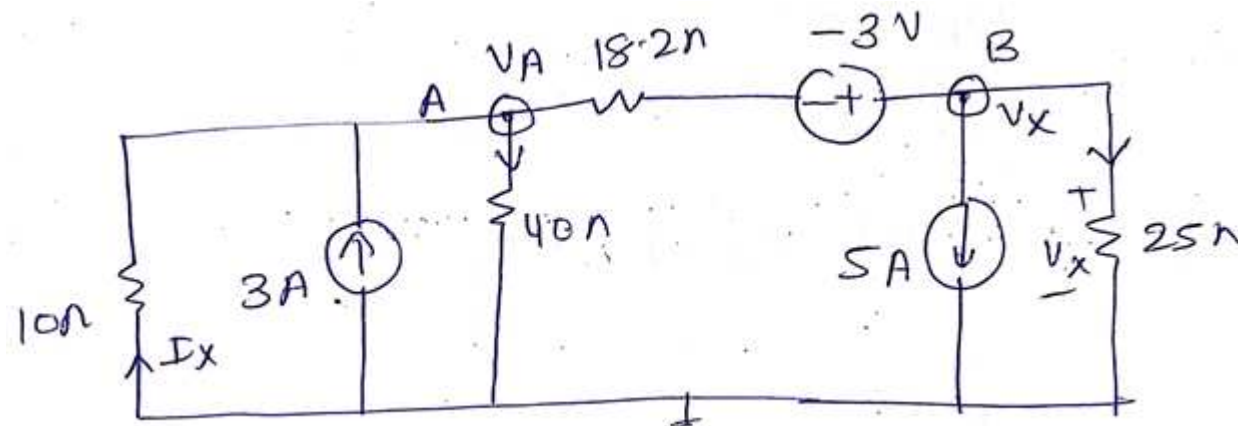

The KCL equation at node 'A':

$$\frac{V_A}{10} + \frac{V_A}{40} + \frac{V_A + (-3) - V_X}{18.2} = 3$$

$$\frac{V_A}{10} + \frac{V_A}{40} + \frac{V_A - 3 - V_X}{18.2} = 3$$

$$0.1V_A + 0.025V_A + 0.055V_A - 0.165 - 0.055V_X = 3$$

$$0.18V_A - 0.055V_X = 3.165 \dots \dots (5)$$

$$0.18V_A = 3.165 + 0.055V_X$$

$$V_A = 17.58 + 0.31V_X \dots \dots (7)$$

The KCL equation at node 'B':

$$\frac{V_X}{25} + 5 + \frac{V_X - (-3) - V_A}{18.2} = 0$$

$$0.04V_X + 5 + 0.0549 V_X + 0.165 - 0.0549V_A = 0$$

$$0.0949V_X - 0.0549V_A = -5.165 \dots \dots (8)$$

Put the equation (7) into (8)

$$0.0949V_X - 0.0549(17.58 + 0.31V_X) = -5.165$$

$$0.0949V_X - 0.965 - 0.0170V_X = -5.165$$

$$0.0779V_X = -4.2$$

$$V_X = -53.92 \text{ V}$$

Likes: 2

Dislikes: 0
