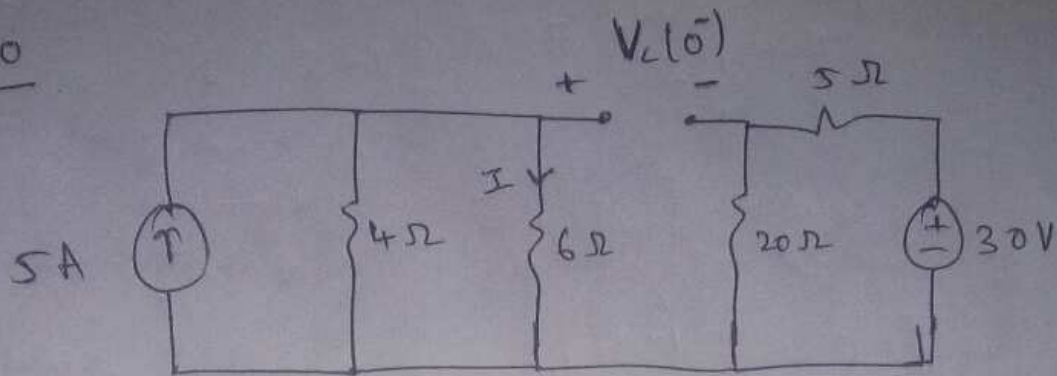


<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)

Answer

$t < 0$



In steady state for $t < 0$ Capacitor will be open circuited.


$$I = 5 \left(\frac{4}{4+6} \right) = 2 \text{ A} \quad V_+ = 6I = 6 \times 2 = 12 \text{ V}$$

$$V_- = 30 \left(\frac{20}{20+5} \right) = 24 \text{ V}$$


$$V_c(0^-) = V_{+-} = V_+ - V_- = 12 - 24 = -12 \text{ V}$$

As Capacitor cannot change its voltage instantaneously $\therefore V_c(0^+) = V_c(0^-) = -12 \text{ V}$

$t > 0$

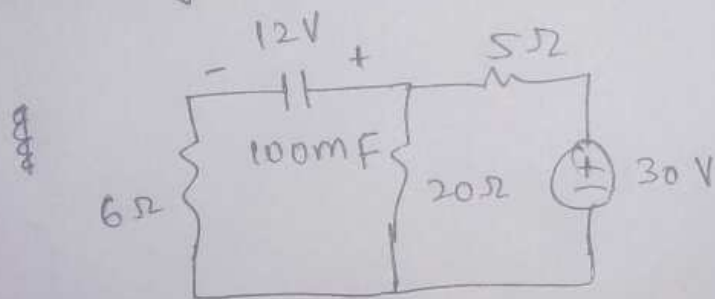

As $t \rightarrow \infty$

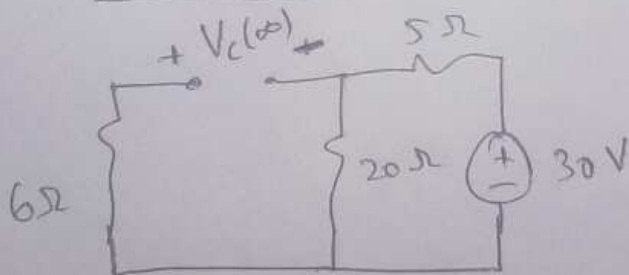

Again in steady state at $t \rightarrow \infty$ C is opened

$$V_c(\infty) = -24 \text{ V}$$

$$V_c(\infty) = -50 \left(\frac{1}{20+5} \right)$$


$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau}$$

$$= -24 + [-12 + 24] e^{-t/\tau}$$

$$V_c(t) = 12(-2 + e^{-t/\tau}) \text{ V}$$

$$\tau = R_{eq} C$$

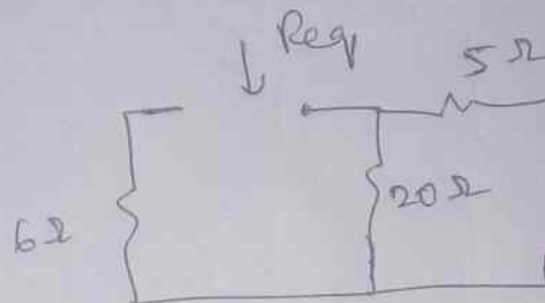R_{eq} is equivalent
resistance seen from
open circuited capacitor with all sources nullified



open circuited capacitor with all sources nullified

$$R_{eq} = 6 + 20 \parallel 5 = 6 + \frac{20 \times 5}{20 + 5} = 10 \Omega$$

~~$$V_c(t) = 12(-2 + e^{-t/10}) \text{ V}$$~~

$$\tau = 10(100 \times 10^{-3}) = 1 \text{ Sec}$$

$$V_c(t) = 12(-2 + e^{-t/1}) \text{ V}$$

$$\boxed{V_c(t) = -24 + 12 e^{-t}} \text{ V for } t > 0$$