

## Solution #2

1. For the circuit in Fig. 1, obtain  $v_1$  and  $v_2$ .

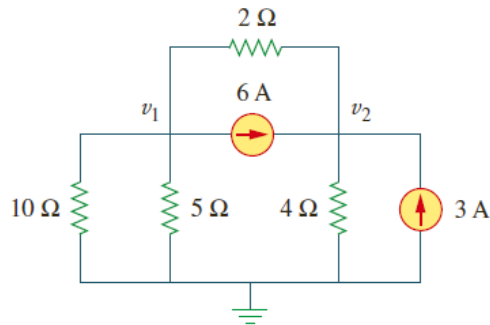


Fig. 1. For Prob. 1.

**Solution:**

At node 1,

$$\frac{-v_1}{10} - \frac{v_1}{5} = 6 + \frac{v_1 - v_2}{2} \rightarrow 60 = -8v_1 + 5v_2 \quad (1)$$

At node 2,

$$\frac{v_2}{4} = 3 + 6 + \frac{v_1 - v_2}{2} \rightarrow 36 = -2v_1 + 3v_2 \quad (2)$$

Solving (1) and (2),

$$v_1 = 0 \text{ V}, v_2 = 12 \text{ V}$$

2. Given the circuit in Fig. 2, calculate the currents  $i_1$  through  $i_4$ . (4%)


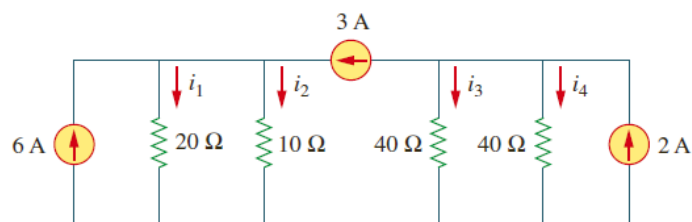


Fig. 2. For Prob. 2.

**Solution:**

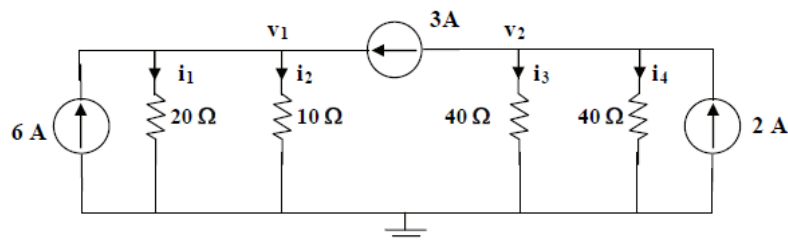

At node 1,

$$-6 - 3 + \frac{v_1}{20} + \frac{v_1}{10} = 0 \rightarrow v_1 = 9 * \left(\frac{20}{3}\right) = 60 \text{ V} \quad (1)$$

At node 2,

$$3 - 2 + \frac{v_2}{40} + \frac{v_2}{40} = 0 \rightarrow v_2 = -1 * \left( \frac{1600}{80} \right) = -20 \text{ V} \quad (2)$$

$$i_1 = \frac{v_1}{20} = 3 \text{ A}, i_2 = \frac{v_1}{10} = 6 \text{ A},$$

$$i_3 = \frac{v_2}{40} = -500 \text{ mA}, i_4 = \frac{v_2}{40} = -500 \text{ mA}.$$

3. Solve for  $V_1$  in the circuit of Fig. 3 using nodal analysis.

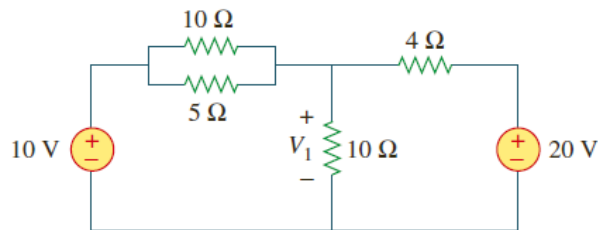


Fig. 3. For Prob. 3.

**Solution:**

Set the bottom of the circuit as the reference node.

At node 1:

$$\begin{aligned} \frac{(V_1 - 10)}{5} + \frac{(V_1 - 10)}{10} + \frac{(V_1 - 0)}{10} + \frac{(V_1 - 20)}{4} &= 0, \\ (0.2 + 0.1 + 0.1 + 0.25)V_1 &= 2 + 1 + 5, \\ V_1 &= 8/0.65 = 160/13 = 12.308 \text{ V}. \end{aligned}$$

4. Using nodal analysis, find  $v_o$  in the circuit of Fig. 4.


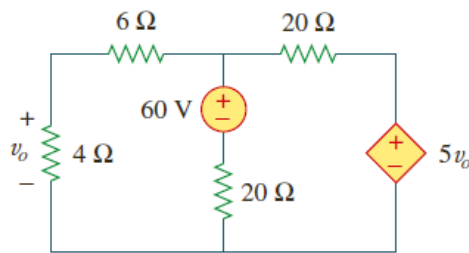


Fig. 4. For Prob. 4.

**Solution:**

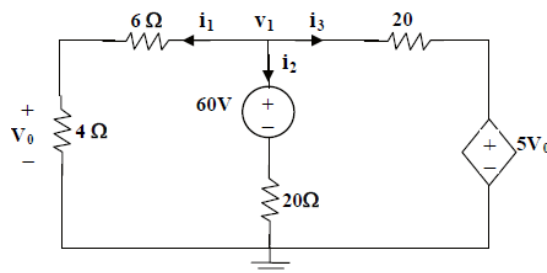

$$i_1 + i_2 + i_3 = 0 \rightarrow \frac{V_1}{10} + \frac{(V_1 - 60) - 0}{20} + \frac{V_1 - 5V_0}{20} = 0$$

But  $V_0 = \frac{2}{5}V_1$ , so that  $2V_1 + V_1 - 60 + V_1 - 2V_1 = 0$

or  $v_1 = 60/2 = 30$  V, therefore  $v_0 = 2v_1/5 = 12$  V.

5. Apply nodal analysis to find  $i_0$  and the power dissipated in each resistor in the circuit of Fig. 5.


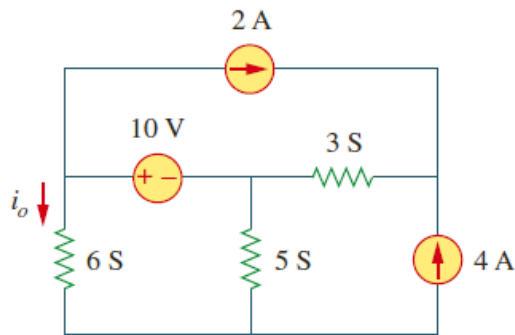


Fig. 5. For Prob. 5.

**Solution:**

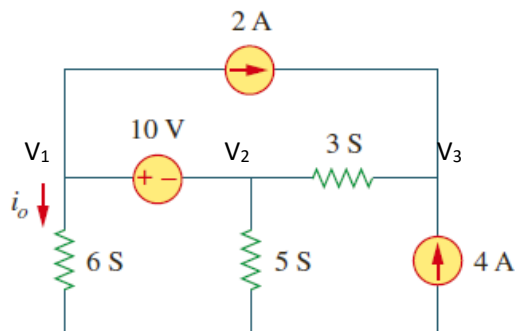

Nodes 1 and 2 form a supernode so that  $v_1 = v_2 + 10$  (1)

At the supernode,  $2 + 6v_1 + 5v_2 = 3(v_3 - v_2) \rightarrow 2 + 6v_1 + 8v_2 = 3v_3$  (2)

At node 3,  $2 + 4 = 3(v_3 - v_2) \rightarrow v_3 = v_2 + 2$  (3)

Substituting (1) and (3) into (2),

$$2 + 6v_2 + 60 + 8v_2 = 3v_2 + 6 \rightarrow v_2 = \frac{-56}{11} = -5.1 \text{ V}$$

$$v_1 = v_2 + 10 = \frac{54}{11} = 4.9 \text{ V}$$

$$i_0 = 6v_1 = 29.45 \text{ A}$$

$$P_{6S} = v_1^2 G = \left(\frac{54}{11}\right)^2 6 = 144.6 \text{ W}$$

$$P_{5S} = v_2^2 G = \left(\frac{-56}{11}\right)^2 5 = 129.6 \text{ W}$$

$$P_{3S} = (v_2 - v_3)^2 G = (2)^2 3 = 12 \text{ W}$$

6. Determine voltages  $v_1$  through  $v_3$  in the circuit of Fig. 6 using nodal analysis.


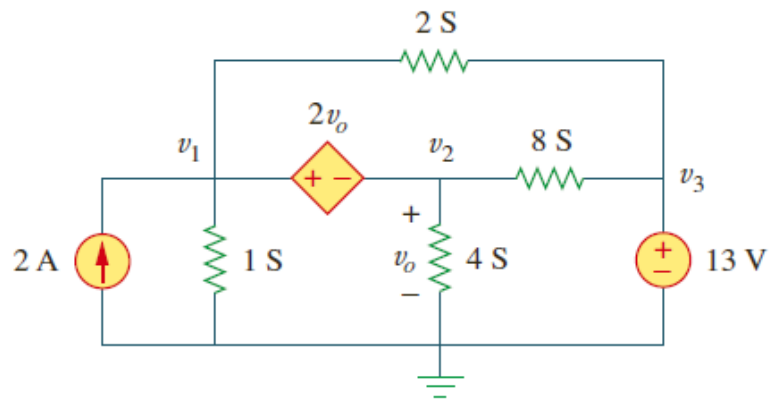


Fig.6. For Prob. 6.

**Solution:**

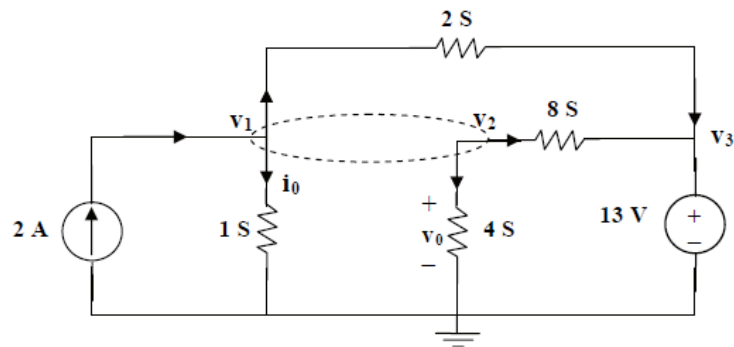

At the supernode,

$$2 = v_1 + 2(v_1 - v_3) + 8(v_2 - v_3) + 4v_2, \text{ which leads to } 2 = 3v_1 + 12v_2 - 10v_3 \quad (1)$$

But  $v_1 = v_2 + 2v_o$  and  $v_o = v_2$ .

$$\text{Hence } v_1 = 3v_2 \quad (2)$$

$$v_3 = 13 \text{ V} \quad (3)$$

Substituting (2) and (3) with (1) gives,  $2 = 9v_2 + 12v_2 - 130$

$$v_1 = 132/7 \text{ V} = \mathbf{18.858 \text{ V}}, \quad v_2 = 44/7 \text{ V} = \mathbf{6.286 \text{ V}}, \quad v_3 = \mathbf{13 \text{ V}}$$

7. Use nodal analysis to find  $v_1$ ,  $v_2$ ,  $v_3$  and in the circuit of Fig. 7.

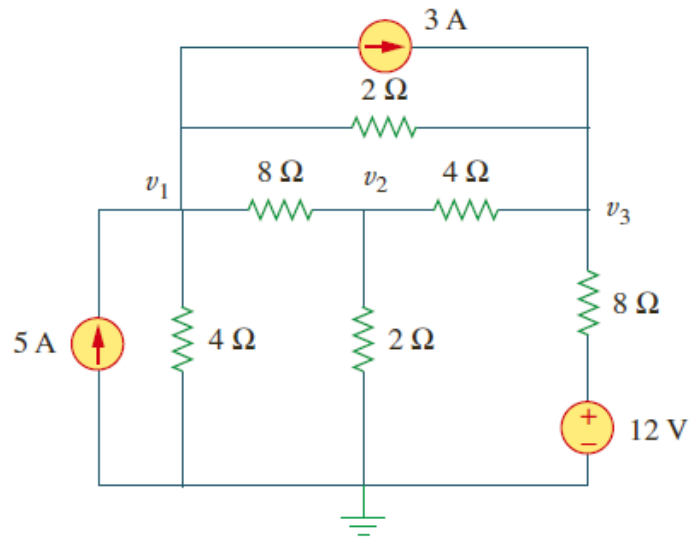


Fig. 7. For Prob. 7.

**Solution:**

At node 1,

$$5 = 3 + \frac{v_1 - v_3}{2} + \frac{v_1 - v_2}{8} + \frac{v_1}{4} \rightarrow 16 = 7v_1 - v_2 - 4v_3 \quad (1)$$

At node 2,

$$\frac{v_1 - v_2}{8} = \frac{v_2 - v_3}{4} + \frac{v_2}{2} \rightarrow 0 = -v_1 + 7v_2 - 2v_3 \quad (2)$$

At node 3,

$$3 + \frac{12 - v_3}{8} + \frac{v_1 - v_3}{2} + \frac{v_2 - v_3}{4} = 0 \rightarrow -36 = 4v_1 + 2v_2 - 7v_3 \quad (3)$$

Form (1) to (3),

$$\begin{pmatrix} 7 & -1 & -4 \\ -1 & 7 & -2 \\ 4 & 2 & -7 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 16 \\ 0 \\ -36 \end{pmatrix} \longrightarrow AV = B$$

Using MATLAB,

$$V = A^{-1}B = \begin{bmatrix} 10 \\ 4.933 \\ 12.267 \end{bmatrix} \longrightarrow \underline{V_1 = 10 \text{ V}, V_2 = 4.933 \text{ V}, V_3 = 12.267 \text{ V}}$$

8. For the circuit in Fig. 8, find  $v_1$ ,  $v_2$  and  $v_3$  using nodal analysis.


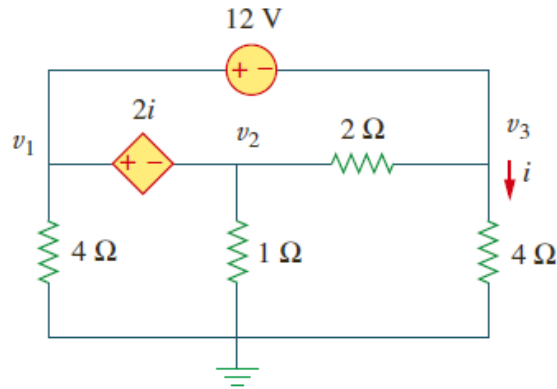


Fig. 8. For Prob. 8.

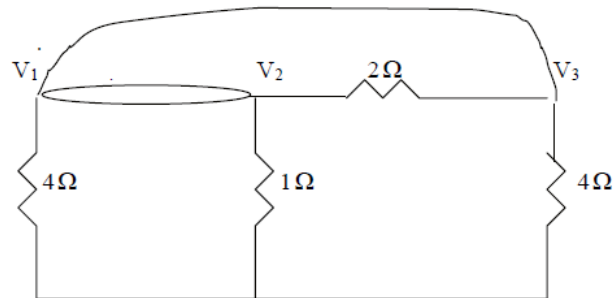**Solution:**

Nodes 1 and 2 form a supernode; so do nodes 1 and 3. Hence

$$\frac{V_1}{4} + \frac{V_2}{1} + \frac{V_3}{4} = 0 \quad \longrightarrow \quad V_1 + 4V_2 + V_3 = 0 \quad (1)$$



Between nodes 1 and 3,

$$-V_1 + 12 + V_3 = 0 \quad \longrightarrow \quad V_3 = V_1 - 12 \quad (2)$$

Similarly, between nodes 1 and 2,

$$V_1 = V_2 + 2i \quad (3)$$

But  $i = V_3 / 4$ . Combining this with (2) and (3) gives

$$V_2 = 6 + V_1 / 2 \quad (4)$$

Solving (1), (2), and (4) leads to

$$\underline{V_1 = -3V, \quad V_2 = 4.5V, \quad V_3 = -15V}$$

9. Use nodal analysis and *MATLAB* to find  $V_0$  in the circuit of Fig. 9.(ML)


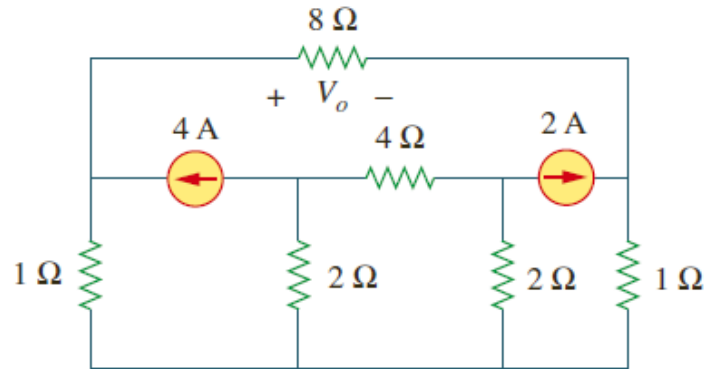


Fig. 9. For Prob. 9.

**Solution:**

Consider the circuit below .

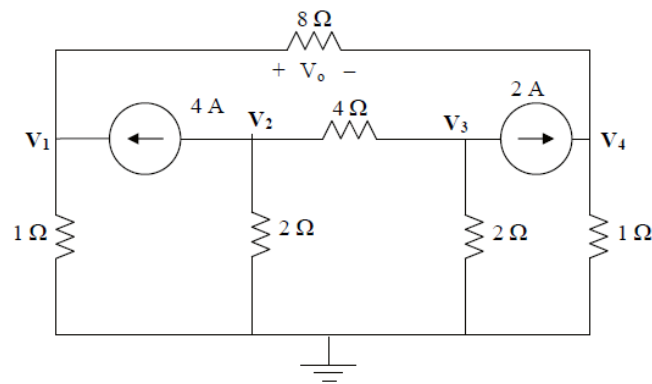

Use nodal analysis at nodes 1~4,

$$\frac{V_1 - 0}{1} - 4 + \frac{V_1 - V_4}{8} = 0 \rightarrow 1.125V_1 - 0.125V_4 = 4 \quad (1)$$

$$+4 + \frac{V_2 - 0}{2} + \frac{V_2 - V_3}{4} = 0 \rightarrow 0.75V_2 - 0.25V_3 = -4 \quad (2)$$

$$\frac{V_3 - V_2}{4} + \frac{V_3 - 0}{2} + 2 = 0 \rightarrow -0.25V_2 + 0.75V_3 = -2 \quad (3)$$

$$-2 + \frac{V_4 - V_1}{8} + \frac{V_4 - 0}{1} = 0 \rightarrow -0.125V_1 + 1.125V_4 = 2 \quad (4)$$

$$\begin{bmatrix} 1.125 & 0 & 0 & -0.125 \\ 0 & 0.75 & -0.25 & 0 \\ 0 & -0.25 & 0.75 & 0 \\ -0.125 & 0 & 0 & 1.125 \end{bmatrix} \mathbf{V} = \begin{bmatrix} 4 \\ -4 \\ -2 \\ 2 \end{bmatrix}$$

Now we can use MATLAB to solve for the unknown node voltage.

```
>> Y=[1.125,0,0,-0.125;0,0.75,-0.25,0;0,-0.25,0.75,0;-0.125,0,0,1.125]
```

Y =

```

1.1250    0    0 -0.1250
0 0.7500 -0.2500    0
0 -0.2500 0.7500    0
-0.1250    0    0 1.1250

```

```
>> I=[4,-4,-2,2]'
```

```
I =
```

```

4
-4
-2
2

```

```
>> V=inv(Y)*I
```

```
V =
```


```

3.8000
-7.0000
-5.0000
2.2000

```

$$V_o = V_1 - V_4 = 3.8 - 2.2 = \mathbf{1.6 \text{ V}}.$$

**10.** Calculate the node voltages  $v_1$ ,  $v_2$ , and  $v_3$  in the circuit of Fig. 10.(ML)

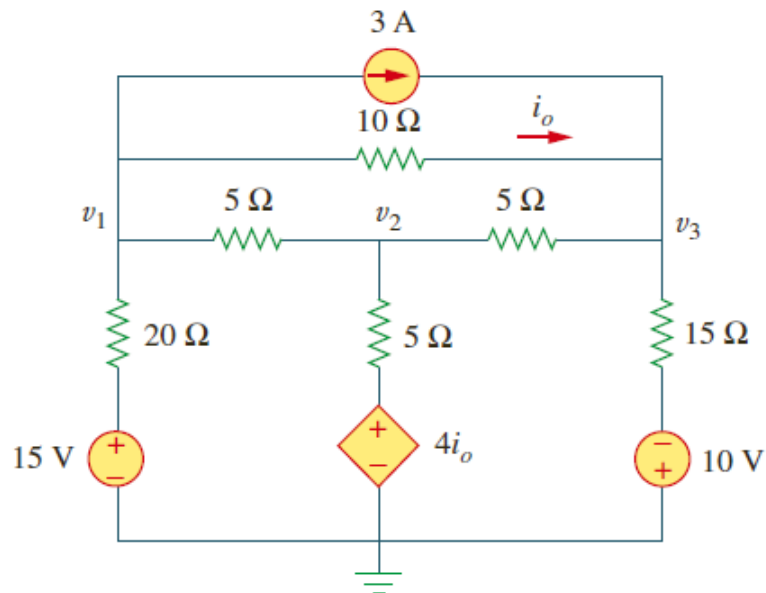

**Fig.10.** For Prob.10.

**Solution:**

At node 1,

$$\frac{15 - V_1}{20} = 3 + \frac{V_1 - V_3}{10} + \frac{V_1 - V_2}{5} \longrightarrow -45 = 7V_1 - 4V_2 - 2V_3 \quad (1)$$

At node 2,



$$\frac{V_1 - V_2}{5} + \frac{4I_o - V_2}{5} = \frac{V_2 - V_3}{5} \quad (2)$$

But  $I_o = \frac{V_1 - V_3}{10}$ . Hence, (2) becomes

$$0 = 7V_1 - 15V_2 + 3V_3 \quad (3)$$

At node 3,

$$3 + \frac{V_1 - V_3}{10} + \frac{-10 - V_3}{15} + \frac{V_2 - V_3}{5} = 0 \longrightarrow 70 = -3V_1 - 6V_2 + 11V_3 \quad (4)$$

Putting (1), (3), and (4) in matrix form produces


$$\begin{pmatrix} 7 & -4 & -2 \\ 7 & -15 & 3 \\ -3 & -6 & 11 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} -45 \\ 0 \\ 70 \end{pmatrix} \longrightarrow AV = B$$

Using MATLAB leads to

$$V = A^{-1}B = \begin{pmatrix} -7.19 \\ -2.78 \\ 2.89 \end{pmatrix}$$

Thus,  $V_1 = -7.19V$ ;  $V_2 = -2.78V$ ;  $V_3 = 2.89V$ .

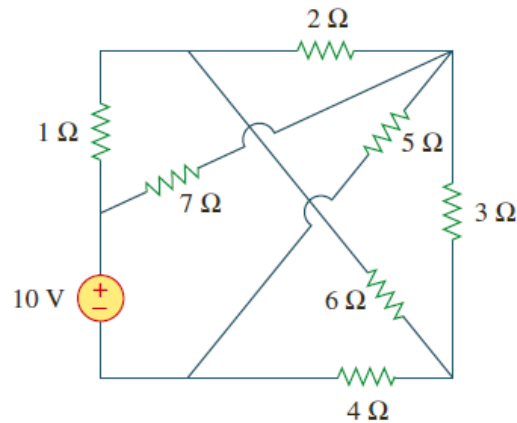**11.** Determine which of the circuits in Fig. 11 is planar and redraw it with no crossing branches.



(a)


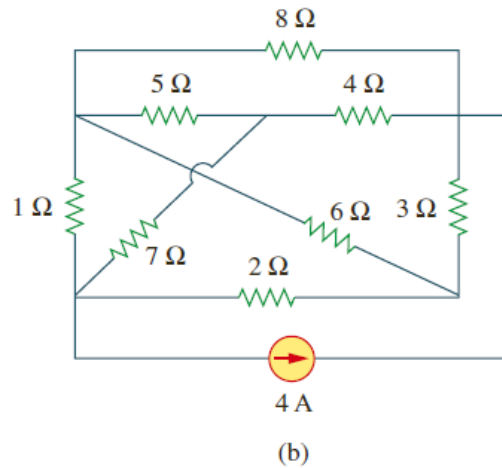



Fig. 11. For Prob. 11.

**Solution:**

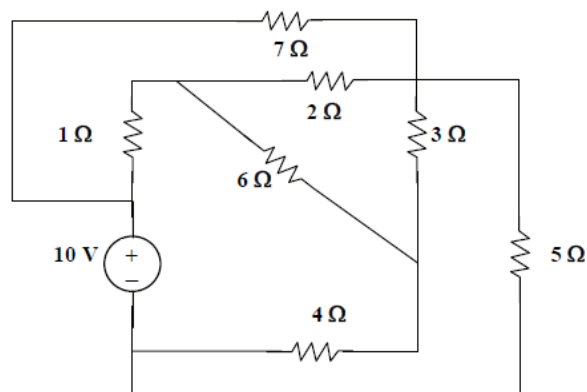(a) This is a planar circuit because it can be redrawn as shown below,



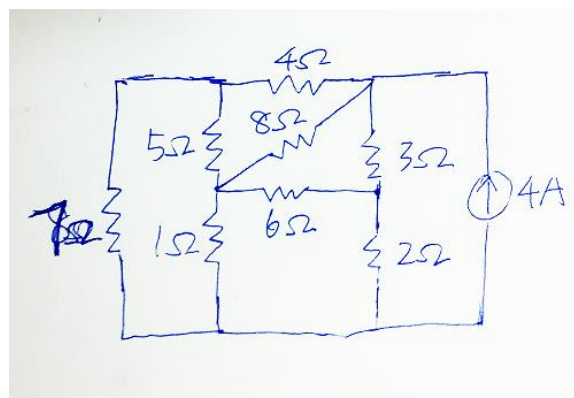(b) This is a planar circuit because it can be redrawn as shown below,



**12.** Apply mesh analysis to the circuit in Fig. 12 and obtain  $I_o$ . (ML)


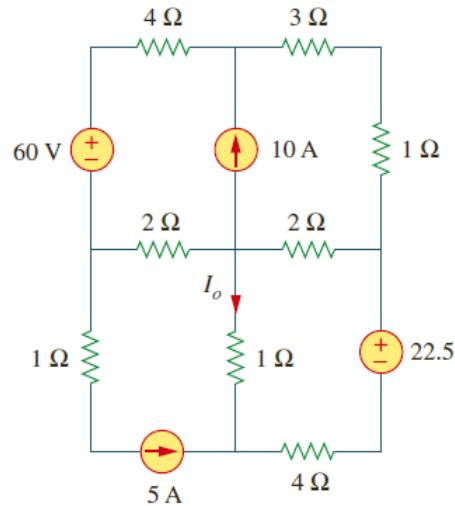


Fig. 12. For Prob.12.

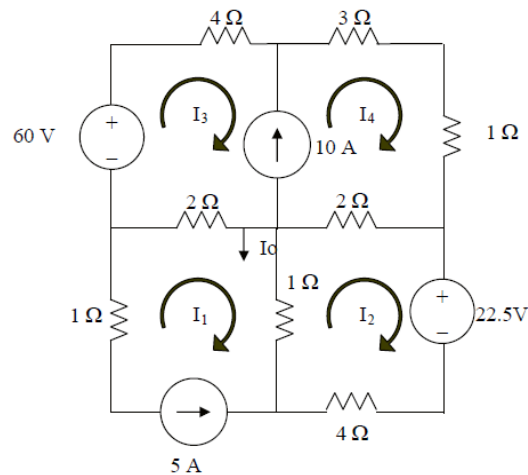**Solution:**

Consider the circuit below with the mesh currents.



$$I_1 = -5A \quad (1)$$

$$1(I_2 - I_1) + 2(I_2 - I_4) + 22.5 + 4I_2 = 0$$

$$7I_2 - 2I_4 = -27.5 \quad (2)$$

$$-60 + 4I_3 + 3I_4 + 1I_4 + 2(I_4 - I_2) + 2(I_3 - I_1) = 0 \text{ super mesh}$$

$$-2I_2 + 6I_3 + 6I_4 = 60 - 10 = 50 \quad (3)$$

But, we need one more equation, so we use the constraint equation  $-I_3 + I_4 = 10$ . This now gives us three equations with three unknowns.

$$\begin{bmatrix} 7 & 0 & -1 \\ -2 & 6 & 6 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -27.5 \\ 50 \\ 10 \end{bmatrix}$$

We can now use MATLAB to solve the problem.

```
>> Z=[7,0,-1;-2,6,6;0,-1,1]
```

$Z =$

```

7   0  -1
-2  6   6
0  -1   0
>> V=[-27.5,50,10]'
```

$V =$

```

-27.5
50
10
>> I=inv(Z)*V
```

$I =$

```

-1.3750
-10.0000
17.8750
```

$$I_0 = I_1 - I_2 = -5 - (-1.375) \text{ A} = -3.625 \text{ A}$$

**13.** For the bridge network in Fig. 13, find  $i_0$  using mesh analysis. (ML)


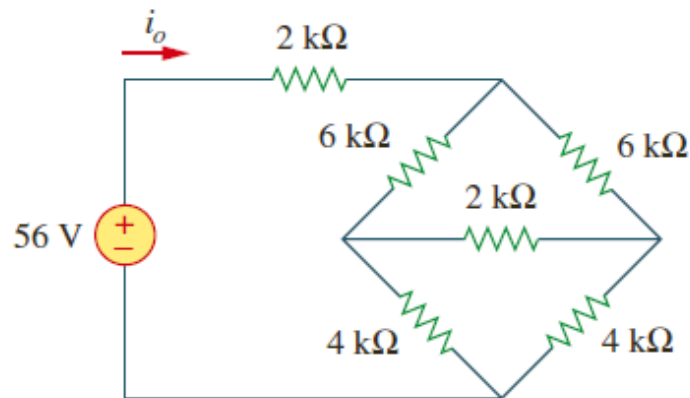


Fig. 13. For Prob.13.

**Solution:**

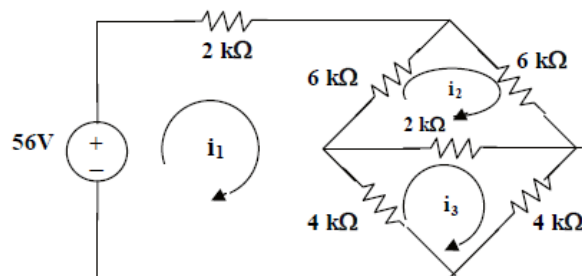

Assume all currents are in mA and apply mesh analysis for mesh 1.

$$-56 + 12i_1 - 6i_2 - 4i_3 = 0 \text{ or } 6i_1 - 3i_2 - 2i_3 = 28 \quad (1)$$

For mesh 2,

$$-6i_1 + 14i_2 - 2i_3 = 0 \text{ or } -3i_1 + 7i_2 - i_3 = 0 \quad (2)$$

For mesh 3,

$$-4i_1 - 2i_2 + 10i_3 = 0 \text{ or } -2i_1 - i_2 + 5i_3 = 0 \quad (3)$$

Solving (1), (2), and (3) using MATLAB, we obtain,

$$i_o = i_1 = \mathbf{8 \text{ mA}}.$$

**14.** Use mesh analysis to obtain  $i_o$  in the circuit of Fig.14.


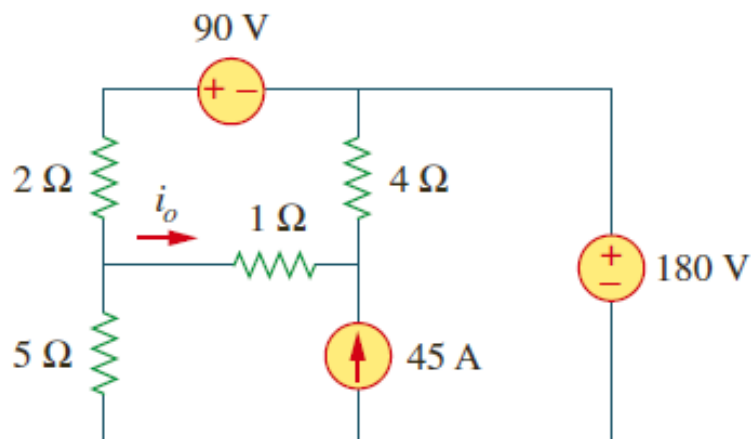


Fig.14. For Prob.14.

**Solution:**

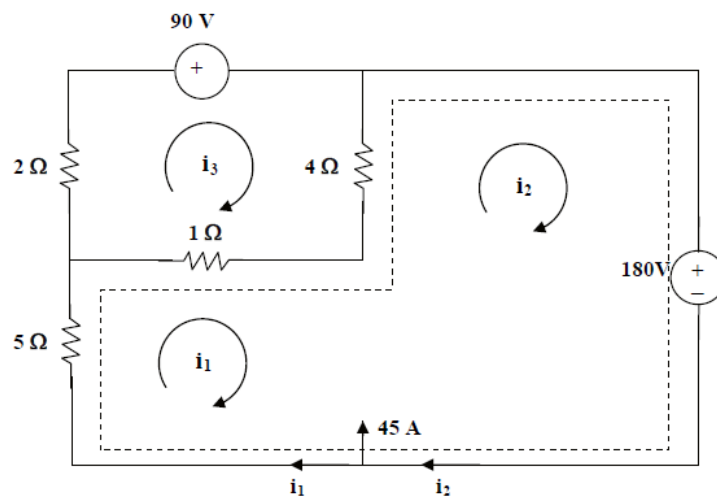

Loop 1 and 2 form a supermesh. For the supermesh,

$$6i_1 + 4i_2 - 5i_3 + 180 = 0 \quad (1)$$

For loop 3,

$$-i_1 - 4i_2 + 7i_3 + 90 = 0 \quad (2)$$

Also,

$$i_2 = 45 + i_1 \quad (3)$$

Solving (1) to (3),

$$i_1 = -46, i_3 = -20; \quad i_0 = i_1 - i_3 = -26 \text{ A}$$

**15.** Use mesh analysis to find the current  $i_0$  in the circuit of Fig. 15. (ML)


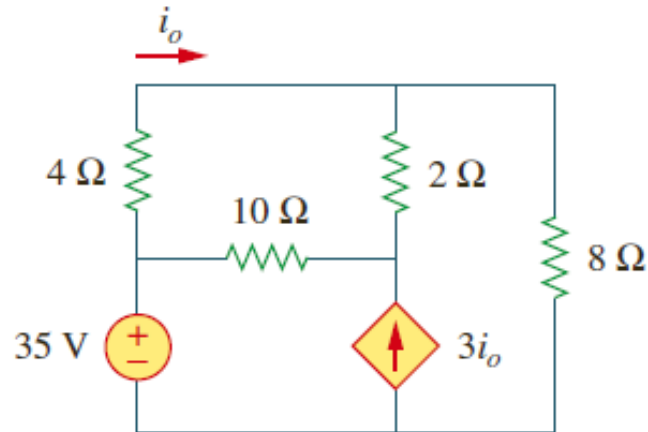


Fig.15. For Prob. 15.

**Solution:**

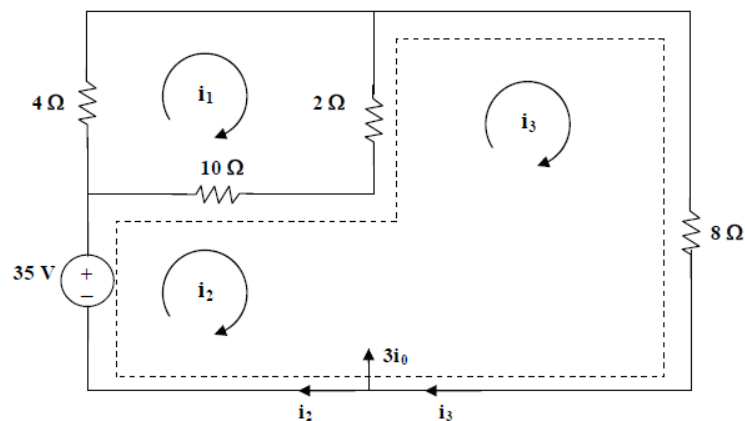

For loop 1,  $16i_1 - 10i_2 - 2i_3 = 0$  which leads to  $8i_1 - 5i_2 - i_3 = 0$  (1)

For the supermesh,  $-35 + 10i_2 - 10i_1 + 10i_3 - 2i_1 = 0$

Or  $-6i_1 + 5i_2 + 5i_3 = 17.5$  (2)

Also,  $3i_0 = i_3 - i_2$  and  $i_0 = i_1$  which leads to  $3i_1 = i_3 - i_2$  (3)

Solving (1), (2), and (3), we obtain  $i_1 = 1.0098$  and

$$i_0 = i_1 = \mathbf{1.0098 \text{ A}}$$

**16.** Find the mesh currents in the circuit of Fig. 16. (ML)

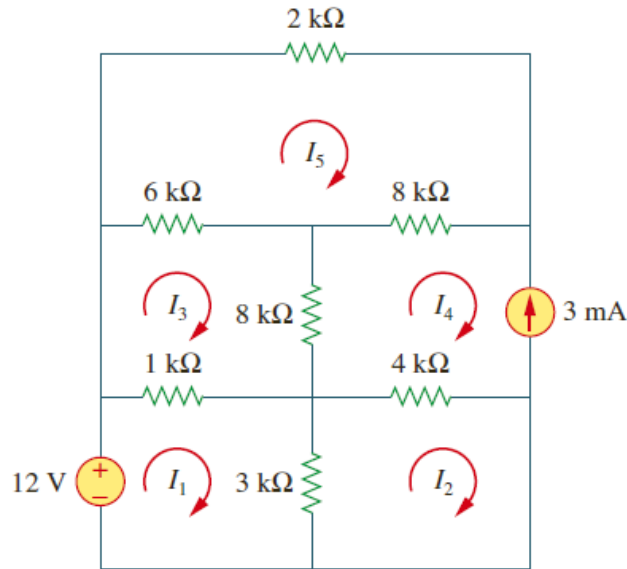


Fig. 16. For Prob. 16.

**Solution:**

Applying mesh analysis leads to;

$$-12 + 4kI_1 - 3kI_2 - 1kI_3 = 0 \quad (1)$$

$$-3kI_1 + 7kI_2 - 4kI_4 = 0 \text{ or } -3kI_1 + 7kI_2 = -12 \quad (2)$$

$$-1kI_1 + 15kI_3 - 8kI_4 - 6kI_5 = 0 \text{ or } -1kI_1 + 15kI_3 - 6k = -24 \quad (3)$$

$$I_4 = -3\text{mA} \quad (4)$$

$$-6kI_3 - 8kI_4 + 16kI_5 = 0 \text{ or } -6kI_3 + 16kI_5 = -24 \quad (5)$$

Putting these in matrix form (having substituted  $I_4 = 3\text{mA}$  in the above),

$$\begin{bmatrix} 4 & -3 & -1 & 0 \\ -3 & 7 & 0 & 0 \\ -1 & 0 & 15 & -6 \\ 0 & 0 & -6 & 16 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_5 \end{bmatrix} = \begin{bmatrix} 12 \\ -12 \\ -24 \\ -24 \end{bmatrix}$$

$$ZI = V$$

Using MATLAB,

```
>> Z = [4,-3,-1,0;-3,7,0,0;-1,0,15,-6;0,0,-6,16]
```

```
Z =
```

```
4 -3 -1 0
```

```
-3 7 0 0
```

```
-1 0 15 -6
```

```
0 0 -6 16
```

```
>> V = [12,-12,-24,-24]'
```

V =  
12  
-12  
-24  
-24

We obtain,  
>> I = inv(Z)\*V

I =  
1.6196 mA  
-1.0202 mA  
-2.461 mA  
-3 mA  
-2.423 mA

17. Find  $v_o$  and  $i_o$  in the circuit of Fig. 17. (ML)


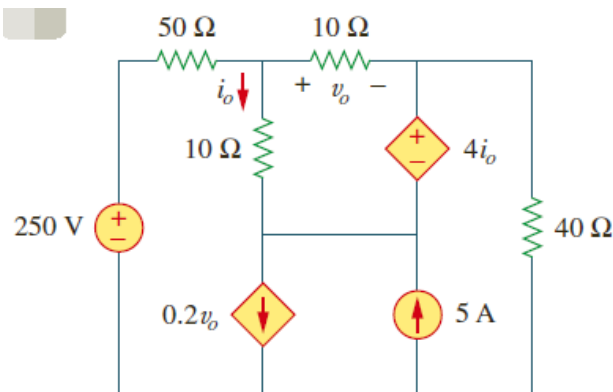


Fig. 17. For Prob. 17.

Solution:

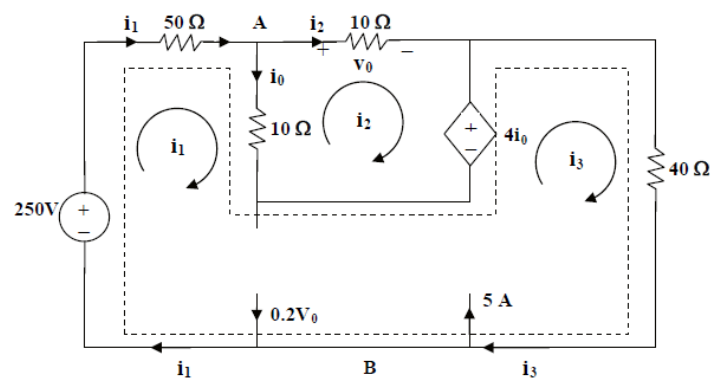

For mesh 2,

$$20i_2 - 10i_1 + 4i_0 = 0 \quad (1)$$

But at node A,  $i_0 = i_1 - i_2$  so that (1) becomes  $i_1 = (16/6)i_2$  (2)

For the supermesh,

$$-250 + 50i_1 + 10(i_1 - i_2) - 4i_0 + 40i_3 = 0 \quad \text{or} \quad 28i_1 - 3i_2 + 20i_3 = 125 \quad (3)$$

At node B,  $i_3 + 0.2v_0 = 2 + i_1$  (4)

But,  $v_0 = 10i_2$ , so that (4) becomes  $i_3 = 5 + (2/3)i_2$  (5)



Solving (1) to (5) ,  $i_2 = 0.2941$  A,

$$v_0 = 10i_2 = \mathbf{2.941 \text{ volts}}, i_0 = i_1 - i_2 = (5/3)i_2 = \mathbf{490.2\text{mA}}.$$

**18.** Write the node-voltage equations by inspection and then determine values of  $V_1$  and  $V_2$  in the circuit of Fig. 18.

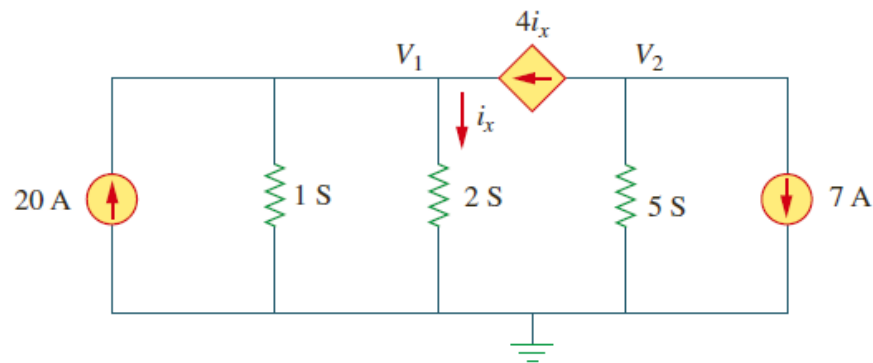


Fig. 18. For Prob. 18.

**Solution:**

$$\begin{bmatrix} 3 & 0 \\ 0 & 5 \end{bmatrix} \mathbf{V} = \begin{bmatrix} 4I_x + 20 \\ -4I_x - 7 \end{bmatrix}$$

With two equations and three unknowns, we need a constraint equation,

$I_x = 2V_1$ , thus the matrix equation becomes,

$$\begin{bmatrix} -5 & 0 \\ 8 & 5 \end{bmatrix} \mathbf{V} = \begin{bmatrix} 20 \\ -7 \end{bmatrix}$$

This results in  $V_1 = 20/(-5) = \mathbf{-4 \text{ V}}$  and  $V_2 = [-8(-4) - 7]/5 = [32 - 7]/5 = \mathbf{5 \text{ V}}$ .

**19.** By inspection, obtain the mesh-current equations for the circuit in Fig. 19.

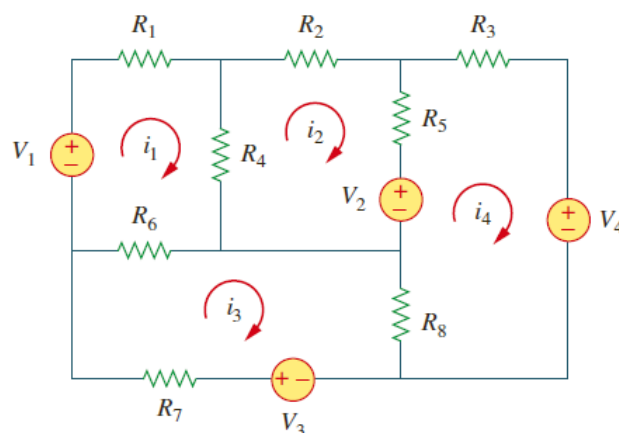


Fig. 19. For Prob. 19.

**Solution:**

$$R_{11} = R_1 + R_4 + R_6, R_{22} = R_2 + R_4 + R_5, R_{33} = R_6 + R_7 + R_8$$

$$R_{44} = R_3 + R_5 + R_8, R_{12} = -R_4, R_{13} = -R_6, R_{14} = 0, R_{23} = 0$$

$R_{24} = -R_5, R_{34} = -R_8$ , again, we note that  $R_{ij} = R_{ji}$  for all  $i$  not equal to  $j$ .

The input voltage vector is

$$= \begin{bmatrix} V_1 \\ -V_2 \\ V_3 \\ V_2 - V_4 \end{bmatrix}$$

$$\begin{bmatrix} R_1 + R_4 + R_6 & -R_4 & -R_6 & 0 \\ -R_4 & R_2 + R_4 + R_5 & 0 & -R_5 \\ -R_6 & 0 & R_6 + R_7 + R_8 & -R_8 \\ 0 & -R_5 & -R_8 & R_3 + R_5 + R_8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \\ V_3 \\ V_2 - V_4 \end{bmatrix}$$

**20.** For the transistor circuit of Fig. 20, find  $v_o$ . Take  $\beta = 200$ ,  $V_{BE} = 0.7$  V.


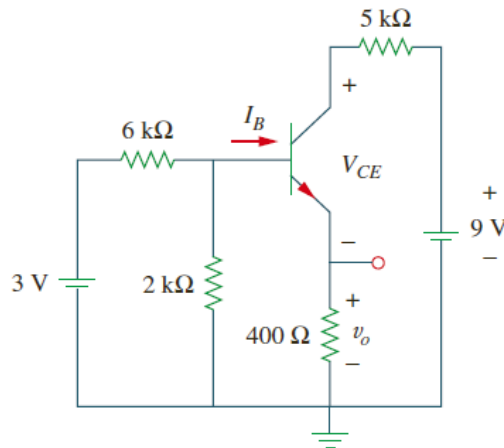


Fig. 20. For Prob. 20.

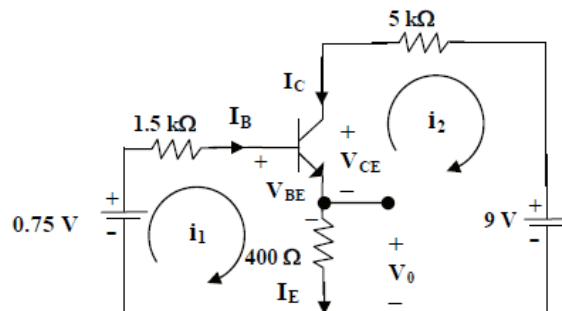**Solution:**

We first determine the Thevenin equivalent for the input circuit.

$$R_{Th} = 6 \parallel 2 = 6 \times 2 / 8 = 1.5 \text{ k} \quad \text{and} \quad V_{Th} = 2(3) / (2+6) = 0.75 \text{ volts}$$



For loop 1,  $-0.75 + 1.5kI_B + V_{BE} + 400I_E = 0 = -0.75 + 0.7 + 1500I_B + 400(1 + \beta)I_B$

$$I_B = 0.05/81,900 = \mathbf{0.61\ \mu A}$$

$$v_0 = 400I_E = 400(1 + \beta)I_B = \mathbf{49\ mV}$$