

<< Search more Solutions!


Found Errors in Solution? >> [Report here!](#)

Answer

7.19

Given circuit

①

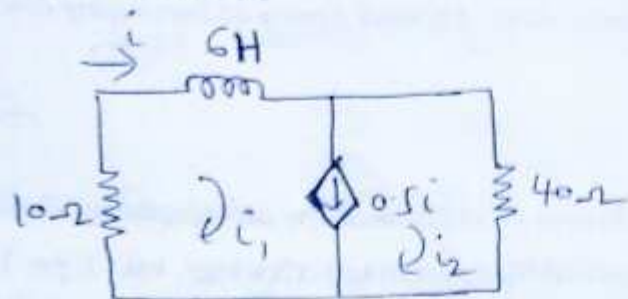

Let us form two loops. By representing two loop currents as shown above

From the circuit $i_1 = i$ — ①

∴ The dependent source of value $0.5i$ is removed in terms of i_1 & i_2 as to form Super-Mesh, $i_1 - i_2 = 0.5i$

$$i_1 - i_2 = 0.5i_1 \quad [\because i = i_1]$$

$$i_2 = 0.5i_1 \quad \text{--- ②}$$

A Super-mesh equation is

$$10i_1 + 6 \frac{di_1}{dt} + 40i_2 = 0$$

$$\text{But } i_1 = i$$

$$10i + 6 \frac{di}{dt} + 40(0.5i_1) = 0 \quad [\because \text{from eq-②}]$$

$$10i + 6 \frac{di}{dt} + 40(0.5i) = 0 \quad [\because \text{from eq-①}]$$

$$6 \frac{di}{dt} + 10i + 20i = 0$$

$$6 \frac{di}{dt} + 30i = 0$$

$$di + 5i = 0 \quad \text{--- ③}$$

It is a

Comparing the above equation with (2)
general first order non-linear differential
equation i.e., $\frac{dy}{dt} + py = q$ whose
solution consists of two parts as

$$y = Ce^{-Pt} + e^{-Pt} \int q e^{Pt} dt$$

Comparing the above eq. to get the
solution for the equation — (3)
we will get

$$i(t) = Ce^{-5t} + e^{-5t} \int 0 e^{5t} dt$$

$$\boxed{i(t) = Ce^{-5t}} \text{ A}$$

The arbitrary constant C in the above
solution can be obtained by applying
initial condition at $t=0^+$

At $t=0^+$, $i(0^+) = 5 \text{ A}$ [Given in the problem]

$$\therefore i(0^+) = Ce^0$$

$$5 = C(1)$$

$$\Rightarrow C = 5$$

$$\therefore \boxed{i(t) = 5e^{-5t}} \text{ A}$$

Likes: 1

Dislikes: 0
