


<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)

## Answer

### Step 1


The given circuit is:

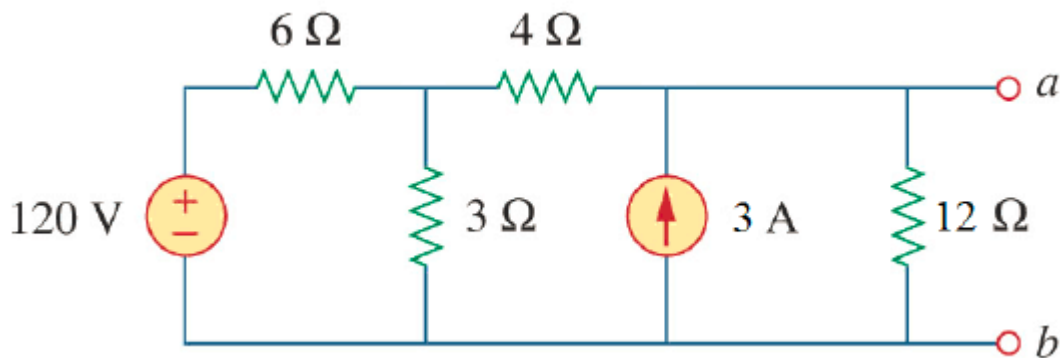

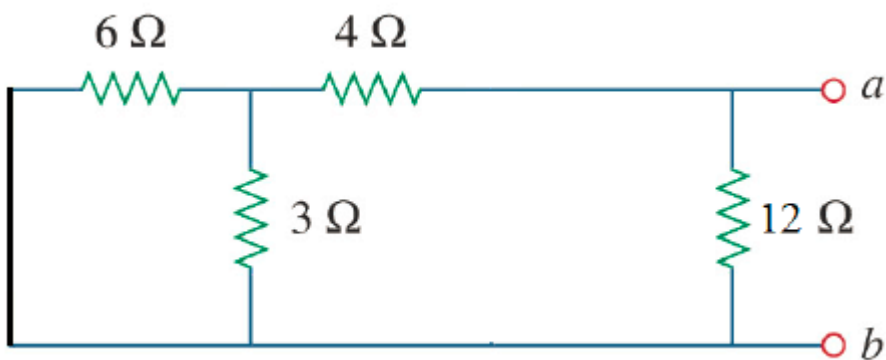
### Step 2


Find Thevenin's equivalent resistance across A and B.

Open circuit the current source and short-circuit the voltage source,




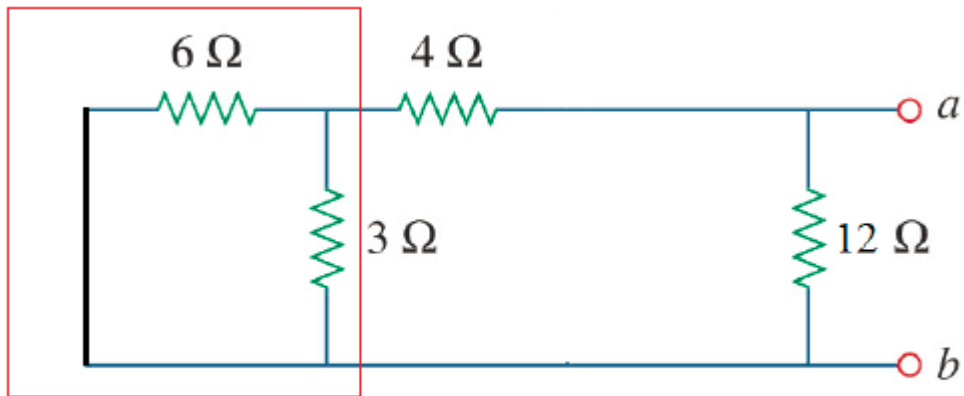

**Parallel,**  
 $6 \parallel 3 = 2$

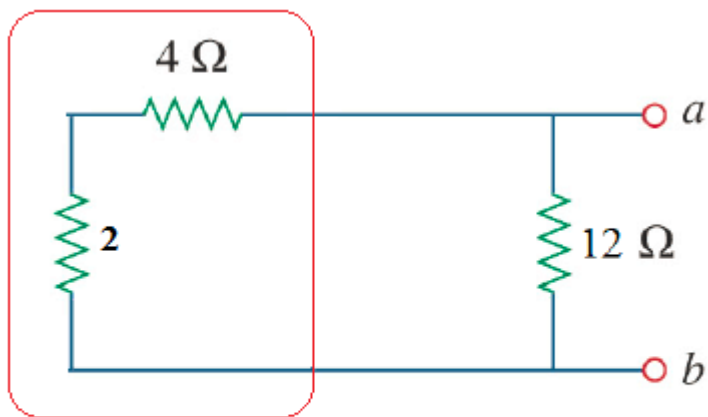

**Series,**  
 $2 + 4 = 6$

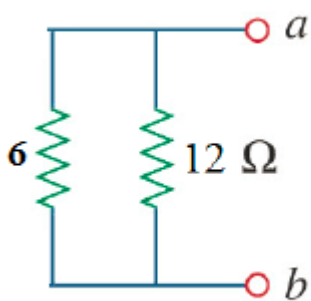


Hence,

$$R_{th} = 6 \parallel 12 = 4\Omega$$

### Step 3

Now find the Thevenin's voltage,

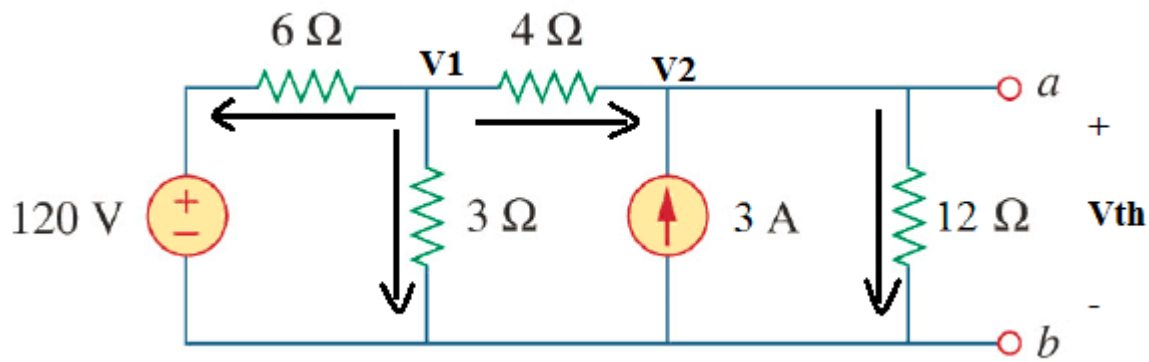

Apply KCL at node  $V_1$ ,

$$\frac{V_1 - 120}{6} + \frac{V_1 - V_2}{4} + \frac{V_1}{3} = 0 \quad 0.75V_1 - 0.25V_2 = 120 \quad \text{--- (1)}$$

Apply KCL at node  $V_2$ ,

$$\frac{V_1 - V_2}{4} + 3 = \frac{V_2}{12} \quad 0.25V_1 - 0.333V_2 = -3 \quad \text{--- (2)}$$

Solve (1) and (2),

$$V_1 = 217.41V \quad V_2 = 172.23V$$

And,

$$V_{th} = V_2 = 172.23V$$

#### Step 4

The Thevenin's equivalent circuit is:

