ID:

Name:

Brac University

Semester: Summer 2023 Course Code: CSE250 Circuits And Electronics

Section: 23 Faculty: PRM





Assessment: Quiz-5 Full Marks: 20

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, the answer script must be returned to the invigilator.
- √ All questions are compulsory. Marks allotted for each question are mentioned beside each question.
- √ Symbols have their usual meanings.

■ Question 1 of 2 [CO3] [5 marks]

Calculate vo(t)


$$\begin{array}{c|c}
60 \Omega \\
\hline
00 \cos(4t - 15^\circ) & + \\
\hline
10 \text{ mF} & 5 \text{ H} & v_o \\
\hline
\end{array}$$

$$\frac{701-15}{700} = \left(\frac{1}{200} + \frac{1}{200}\right) = \frac{1000}{1000} = \frac{50}{1000}$$

$$-1.V_0 = \frac{2p}{60+2p} \times 202-15^\circ = 17.15 L 15.96^\circ V$$

■ Question 2 of 2 [CO3] [15 marks]

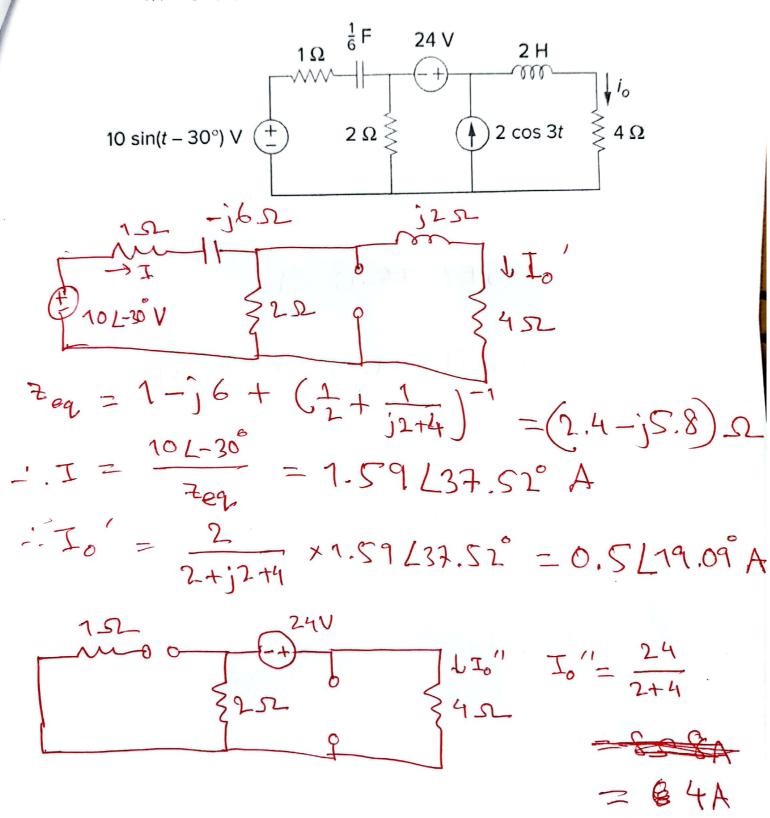Calculate i_o(t) using Superposition Principle.



$$\frac{12}{100} - \frac{1}{100}$$

$$\frac{1}{100} = \frac{1}{100}$$

$$\frac{1}{100} = \frac{1}{100}$$

$$\frac{1}{100} + \frac{1}{100} + \frac{1}{100}$$

= 0.34 L-76.43° A

$$a(t) = 0.5 \sin(t + 19.09) + 4 + 0.34 \cos(3t - 76.43)$$