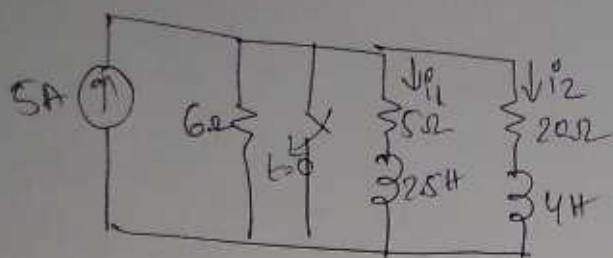


<< Search more Solutions!

**Found Errors in Solution? >> [Report here!](#)**

**Answer**

7.57) Find  $i_1(t)$  &  $i_2(t)$  for  $t > 0$  in the circuit. Page No. (1)




Current through the inductor

$$i(t) = (i(\infty) - i(\infty))e^{-t/\tau} + i(\infty) \quad t > 0.$$

for  $t < 0$ , circuit is under steady state condition

Inductors  $\rightarrow$  Short circuited.

Switch  $\rightarrow$  open.

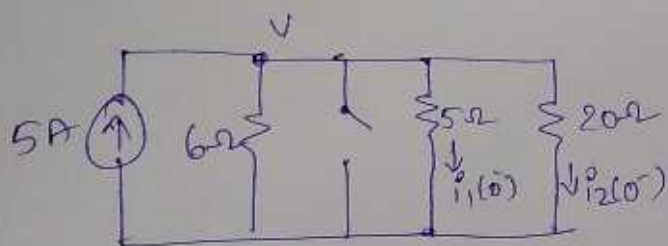

By nodal analysis

$$5 = \frac{V}{6} + \frac{V}{5} + \frac{V}{20}$$

$$5 = \frac{10V + 12V + 3V}{60}$$

$$\Rightarrow 300 = 25V$$

$$\Rightarrow V = \frac{12 \times 300}{25} \Rightarrow V = 12 \text{ volts}$$

Therefore,

$$i_1(0) = \frac{V}{5} = \frac{12}{5} = 2.5 \text{ A}$$

$$i_2(0) = \frac{V}{20} = \frac{12}{20} = 0.6 \text{ A}$$

As we know inductor doesn't allow sudden changes in current.


So,  $i_1(0) = i_1(0^-) = i_1(0)$

$$i_1(0) = i_1(0^-) = 2.5 \text{ A}$$

$$i_2(0) = i_2(0^-) = 0.6 \text{ A}$$

at  $t = \infty$ , circuit becomes

page no (2)

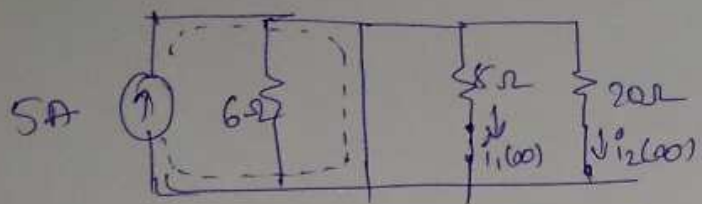

here total current is diverted through short circuited path. Hence  $i_1(\infty) = i_2(\infty) = 0$

Time-constant for  $i_1 \Rightarrow \tau_1 = L/R_1 = \frac{2.5}{50} = \frac{1}{2}$

Time-constant for  $i_2 \Rightarrow \tau_2 = L/R_2 = \frac{41}{205} = \frac{1}{5}$

therefore

$$i_1(t) = (i_1(0) - i_1(\infty)) e^{-t/\tau_1} + i_1(\infty)$$

$$= (2.5 - 0) e^{-t/1/2} + 0$$

$$i_1(t) = 2.5 e^{-2t} \text{ A } t > 0$$

$$i_2(t) = (i_2(0) - i_2(\infty)) e^{-t/\tau_2} + i_2(\infty)$$

$$= (0.6 - 0) e^{-t/1/5} + 0$$

$$i_2(t) = 0.6 e^{-5t} \text{ A } t > 0$$