

<< Search more Solutions!

**Found Errors in Solution? >> [Report here!](#)**

## **Answer**


**ANSWER :**

**GIVEN THAT :**

at  $t = 0^-$  (steady state)


switch is open

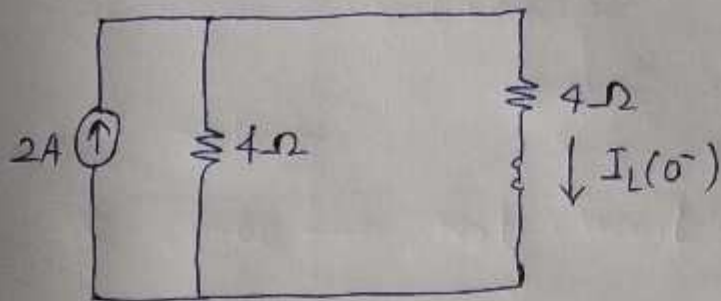Inductor  $\rightarrow$  short circuit      short




$$I_L(0^-) = I_L(0^+) = 2 \times \frac{4}{4+4} = 1A \quad \left[ \begin{array}{l} \text{Current} \\ \text{division} \end{array} \right]$$

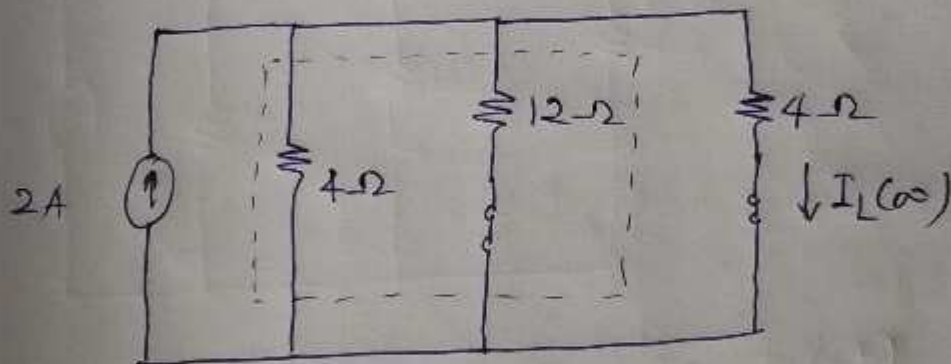At  $t = \infty \Rightarrow$  switch is ON  
Inductor  $\rightarrow$  short circuit



$$4 \parallel 12 = \frac{4 \times 12}{4 + 12} = 3\Omega$$

$\hookrightarrow$  in parallel

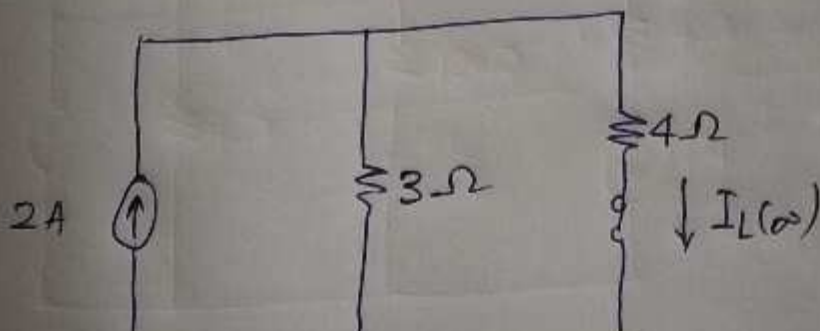




$$I_L(\infty) = 2 \times \frac{3}{3+4} = 2 \times \frac{3}{7} = \frac{6}{7} \text{ A}$$

$$\tau = \text{time constant} = \frac{L}{R_{eq}}$$

$R_{eq}$ :

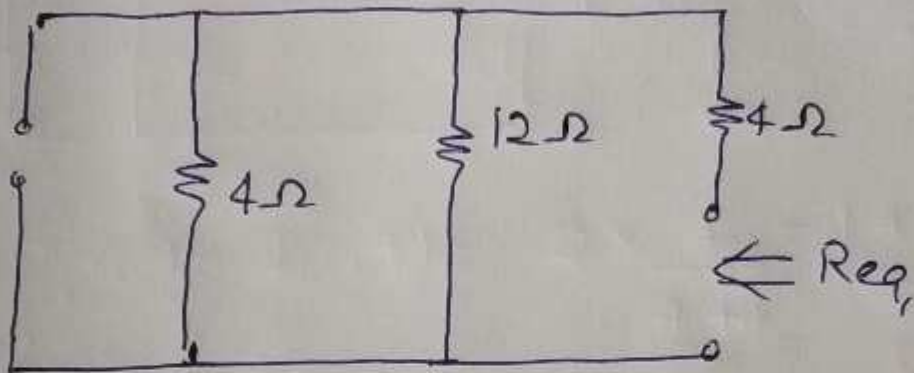

$$R_{eq} = [4 \parallel 12] + 4 = \left[ \frac{4 \times 12}{4 + 12} \right] + 4$$

$$= 7\Omega$$

$$i(t) = I_L(\infty) + [I_L(0^+) - I_L(\infty)] e^{-t/\tau}$$

$$= \frac{6}{7} + \left[ 1 - \frac{6}{7} \right] e^{-t \times \frac{7}{3.5}}$$


$$\therefore i(t) = \frac{6}{7} + \frac{1}{7} e^{-2t} ; t \geq 0$$



b) At  $t = 0^-$  (steady state)

Switch  $\rightarrow$  open

Inductor  $\rightarrow$  short circuit

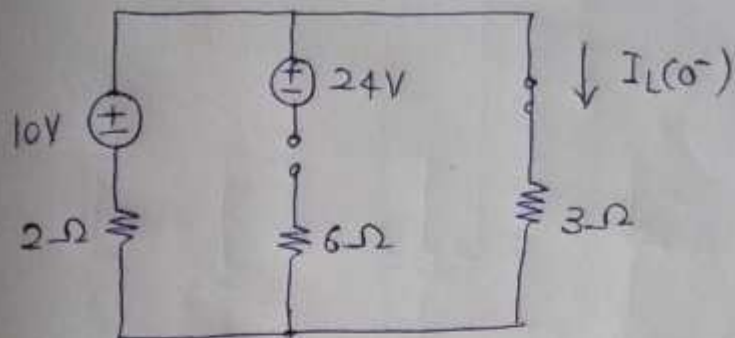


$$I_L(0^-) = I_L(0^+) = \frac{10}{5} = 2 \text{ A}$$

At  $t = \infty$  (steady state)

Switch  $\rightarrow$  close

Inductor  $\rightarrow$  short circuit

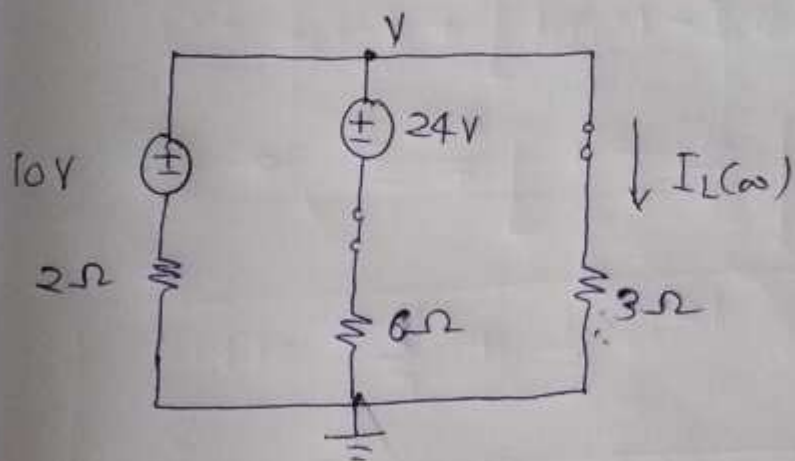

KCL at Node-V

$$\frac{V - 10}{2} + \frac{V - 24}{6} + \frac{V}{3} = 0$$


$$V = \frac{10}{2} + \frac{24}{6} = 9 \text{ V}$$

$$I_L(\infty) = 9 = 3 \text{ A}$$

$$i(t) = I_L(\infty) + [I_L(0^+) - I_L(\infty)] e^{-t/\tau}$$

$$\tau = \frac{L}{R_{eq}}$$

$R_{eq}$ :

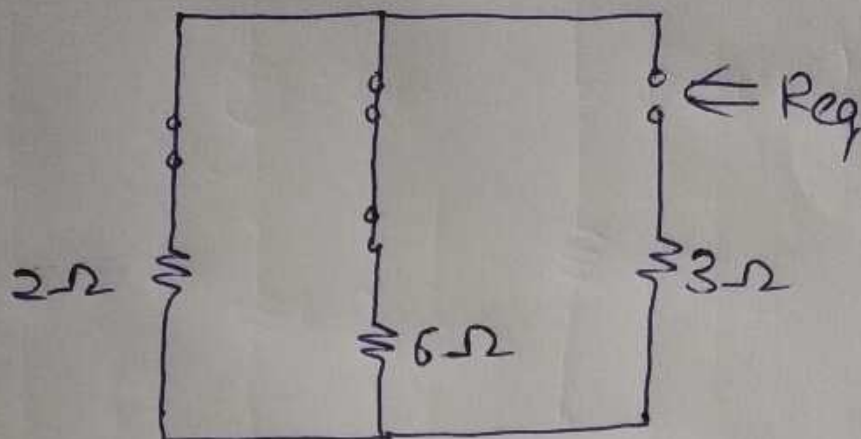

$$\begin{aligned} R_{eq} &= 3 + [2 \parallel 6] \\ &= 3 + \left[ \frac{2 \times 6}{2 + 6} \right] = \frac{9}{2} \end{aligned}$$

$$\tau = \frac{2}{\frac{9}{2}} = 2 \times \frac{2}{9} = \frac{4}{9}$$

$$i(t) = 3 + [2 - 3] e^{-\frac{9}{4}t}; t \geq 0$$

**Likes: 3**

**Dislikes: 0**

---