

<< Search more Solutions!




**Found Errors in Solution? >> [Report here!](#)**

## **Answer**

As you have posted multiple questions at once Homework Help policy allows to answer only the first question.

2)

②

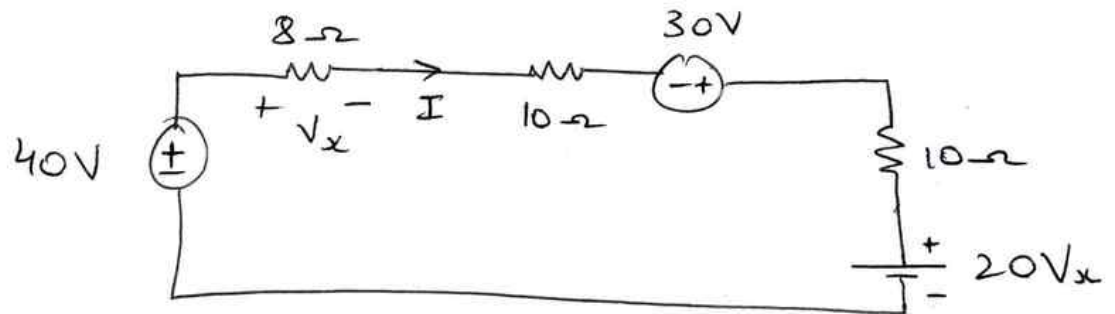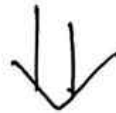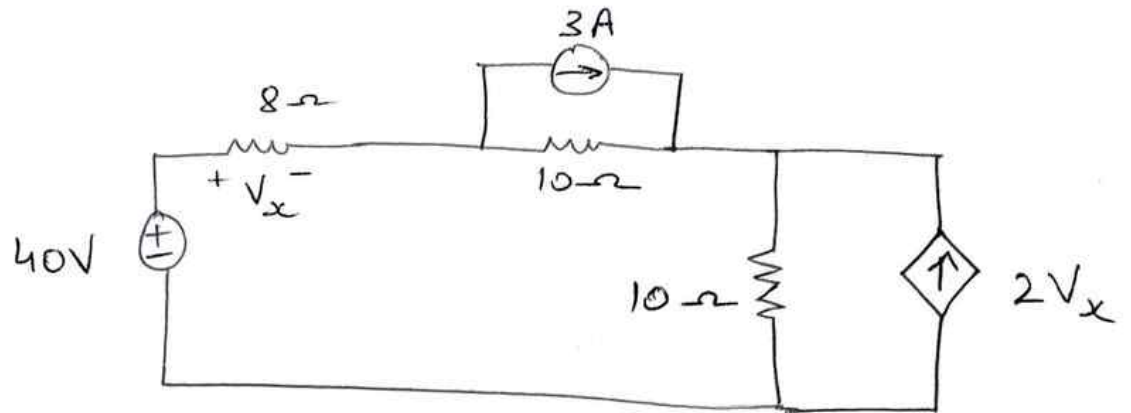

$$\frac{40 - V_x + 30 - 20V_x}{20} = I$$

$$\Rightarrow \frac{70 - 21V_x}{20} = \frac{V_x}{8}$$

$$\Rightarrow \boxed{V_x = 3.11 \text{ V}}$$

Likes: 0

Dislikes: 0