

ID:

Name:

Brac University

Semester: Summer 2023

Course Code: CSE250

Circuits And Electronics

Section: 23

Faculty: PRM




Inspiring Excellence

Assessment: Assignment-4


- ✓ Submit softcopy online by deadline
- ✓ Submit hardcopy in class by deadline

■ Question 1 of 3 [CO1] [10 marks]

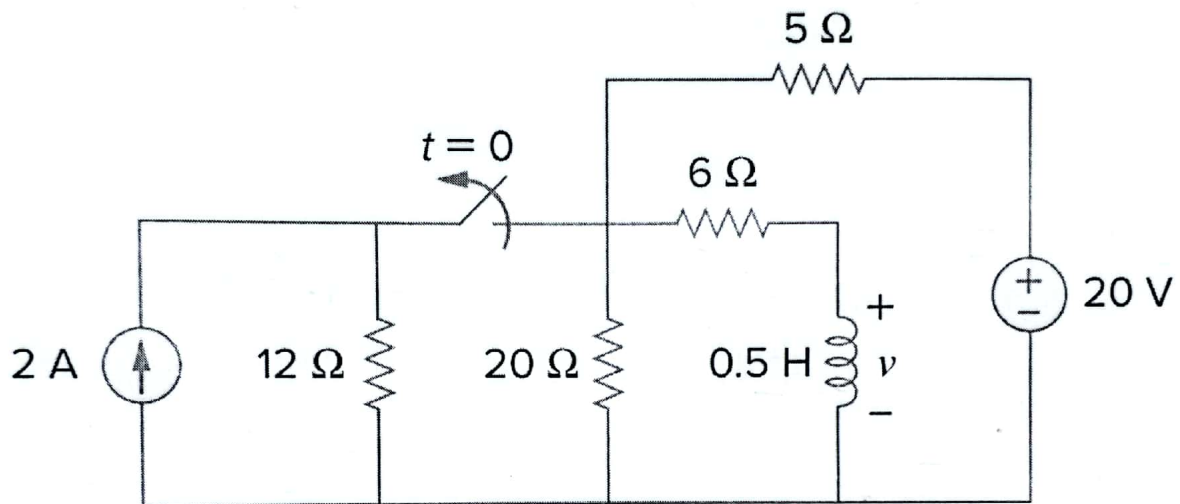Determine $v(t)$ and $i_L(t)$ for $t < 0$ and $t > 0$.



for $t < 0$,

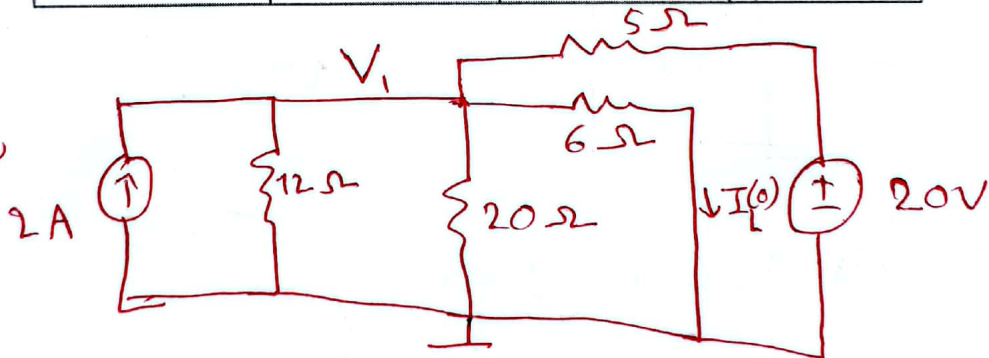

$$-2 + \frac{V_1}{12} + \frac{V_1}{20} + \frac{V_1}{6} + \frac{V_1 - 20}{5} = 0$$


$$\therefore V_1 = 12 \text{ V}$$

$$\therefore I_L(0) = i_L(0) = \frac{V_1}{6} = 2 \text{ A}$$

$$v(0) = 0 \text{ V}$$

for $t > 0$,


For $t > 0$,

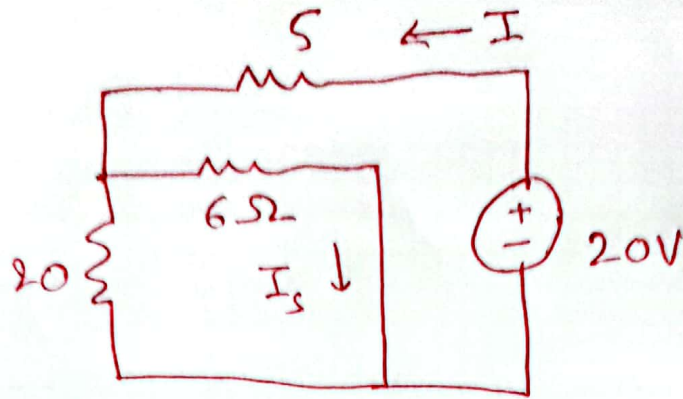

$$R_{eq} = 5 + \left(\frac{1}{20} + \frac{1}{6} \right)^{-1} = 9.62 \Omega$$

$$I = \frac{20}{R_{eq}} = 2.08 \text{ A}$$
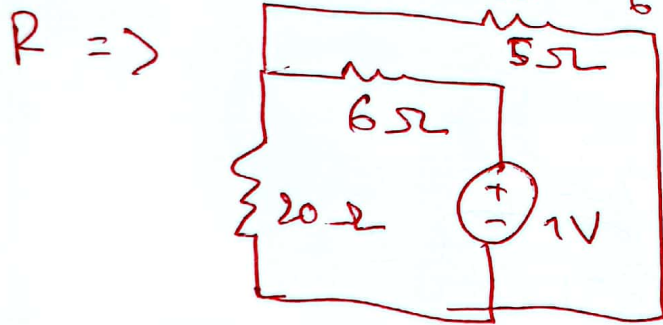
$$I_s = i_L(\alpha) = \frac{\frac{1}{6}}{\frac{1}{20} + \frac{1}{6}} \times 2.08 = 1.6 \text{ A}$$



$$R = 6 + \left(\frac{1}{20} + \frac{1}{5} \right)^{-1} = 10 \Omega$$




$$\therefore i_L(t) = 1.6 + (2 - 1.6)e^{-\frac{10t}{0.5}} = 1.6 + 0.4e^{-20t}$$

$$v(t) = L \frac{di_L(t)}{dt} = -4e^{-20t}$$

$$\therefore i_L(t) = \begin{cases} 2, & t \leq 0 \\ 1.6 + 0.4e^{-20t}, & t > 0 \end{cases}$$

$$v(t) = \begin{cases} 0, & t \leq 0 \\ -4e^{-20t}, & t > 0 \end{cases}$$

Question 2 of 3 [CO1] [10 marks]

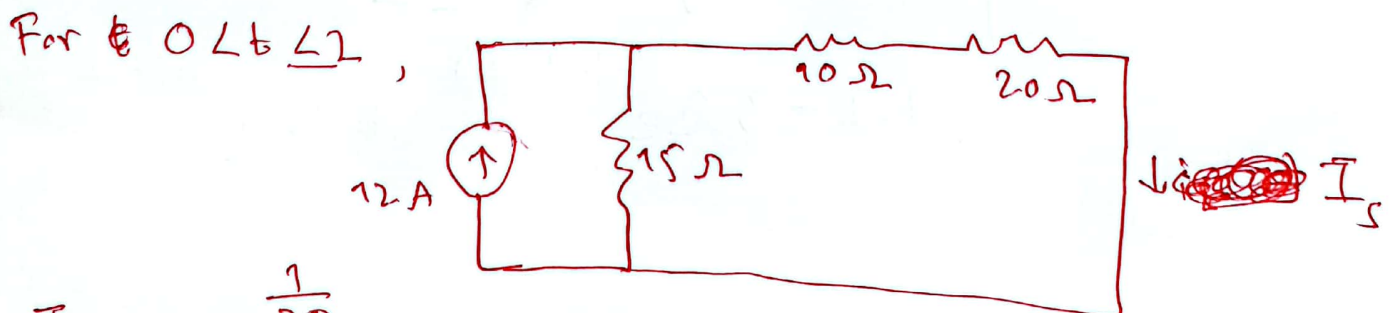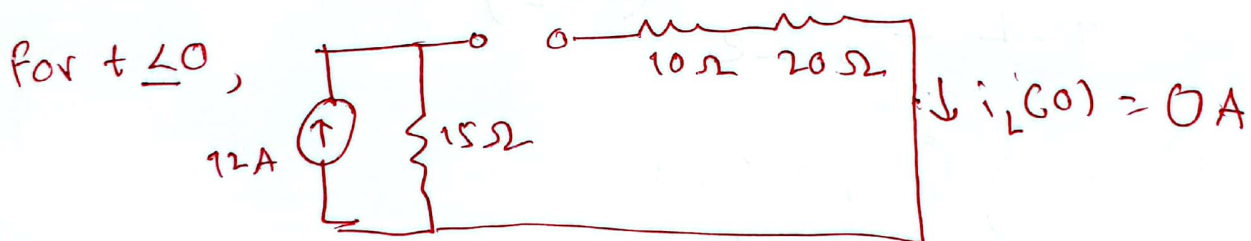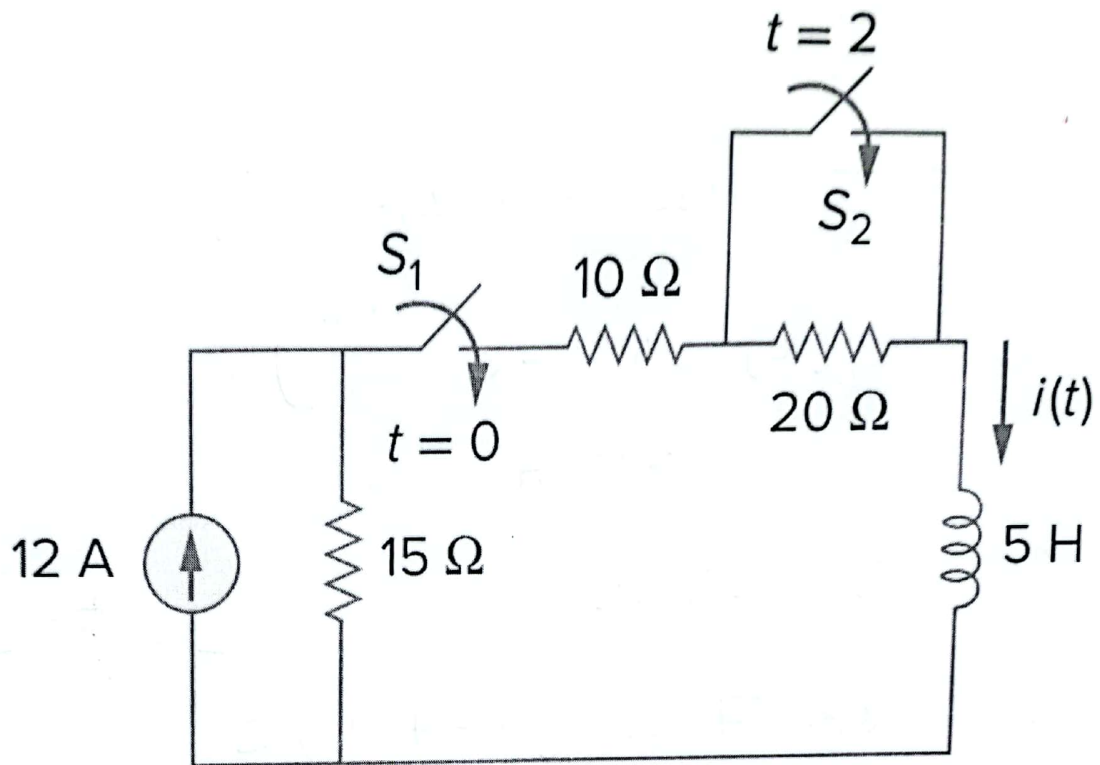
Determine $i(t)$ for $t < 0$, $t > 0$ and $t > 2$.

$$I_s = \frac{\frac{1}{30}}{\frac{1}{15} + \frac{1}{30}} \times 12 = 4 \text{ A}$$

$$R = 10 + 20 + 15 = 45 \Omega$$

$$\therefore i_L(t) = 4 - 4e^{-\frac{45t}{5}} = 4(1 - e^{-9t}) \text{ A}$$

For $t > 2$,

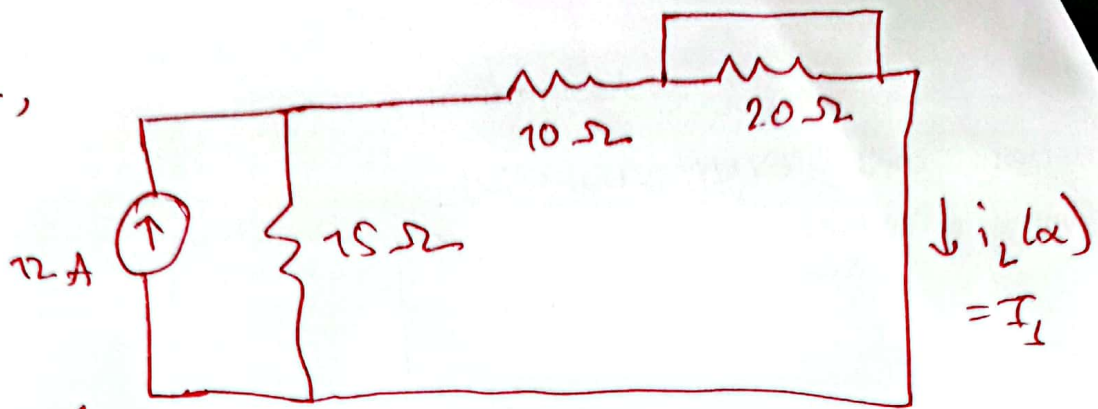

$$i_L(\infty) = \frac{\frac{1}{10}}{\frac{1}{15} + \frac{1}{10}} \times 12 = 7.2 \text{ A} = I_S$$

$$\text{Here, } I_0 = i_L(2) = 4(1 - e^{-9 \times 2}) \approx 4 \text{ A}$$




$$R = 10 + 15 = 25\Omega$$

$$= \frac{25(t-2)}{5}$$

$$\therefore i_L(t) = 7.2 + (4 - 7.2)e^{-5(t-2)} = 7.2 - 3.2e^{-5(t-2)}$$

$$\therefore i_L(t) = \begin{cases} 0, & t \leq 0 \\ 4(1 - e^{-9t}), & 0 \leq t \leq 2 \\ 7.2 - 3.2e^{-5(t-2)}, & t > 2 \end{cases}$$

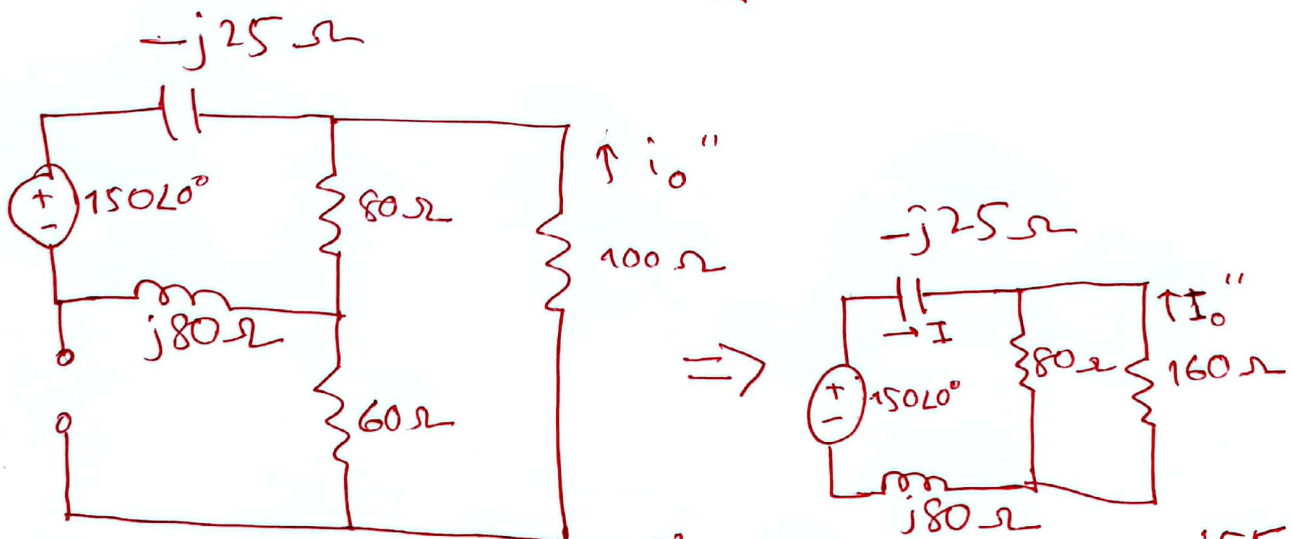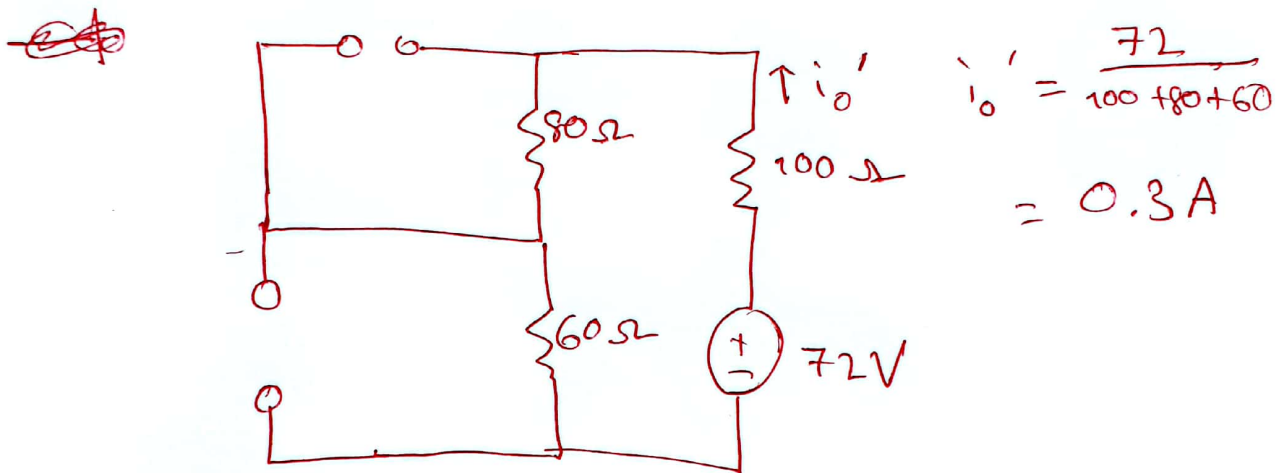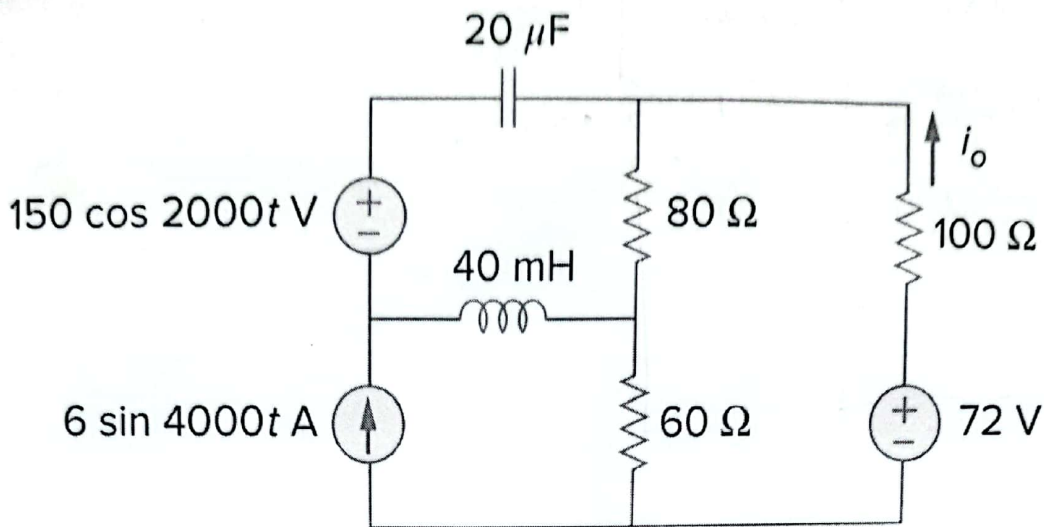Question 3 of 3 [CO1] [10 marks]
Determine $i_o(t)$.



$$Z_{eq} = -j25 + \left(\frac{1}{\frac{1}{80} + \frac{1}{160}} \right) + j80 = 53.33 + j55$$

$$I_1 = \frac{150 \angle 0^\circ}{Z_{eq}} = \frac{150 \angle 0^\circ}{53.33 + j55} = 1.96 \angle -45.88^\circ \text{ A}$$

$$I_o'' = -\frac{80}{80 + 160} I_1 = 0.65 \angle 134.12^\circ \text{ A}$$