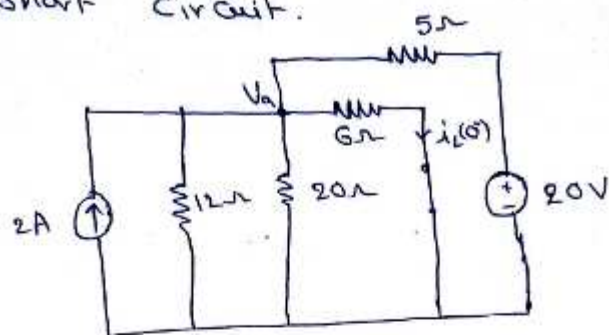


<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)

Answer

from $t = -\infty$ to $t = 0^-$ switch is closed, inductor acts as short circuit.



Apply nodal analysis at V_a

$$-2 + \frac{V_a}{12} + \frac{V_a}{20} + \frac{V_a}{6} + \frac{V_a - 20}{5} = 0$$


$$V_a \left[\frac{1}{12} + \frac{1}{20} + \frac{1}{6} + \frac{1}{5} \right] = 6$$

$$\boxed{V_a = 12V}$$

$$\therefore i_L(0^-) = i_L(0^+) = \frac{V_a}{6} = \frac{12}{6}$$

$$\boxed{i_L(0^+) = 2A}$$

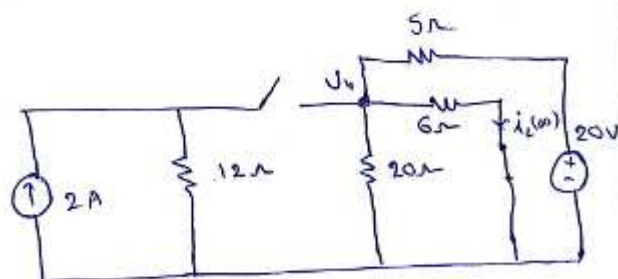at $t = 0$ switch is open, at $t = \infty$ inductor acts as short circuit.



Apply nodal analysis at V_b

$$\frac{V_b}{20} + \frac{V_b}{6} + \frac{V_b - 20}{5} = 0$$

$$V_b \left[\frac{1}{20} + \frac{1}{6} + \frac{1}{5} \right] = 4$$

$$V_b = 9.6V$$

$$\therefore i_L(\infty) = \frac{V_b}{G} = 1.6 \text{ A.}$$

for $t > 0$

$$\therefore i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)] e^{-t/\tau}$$

$$\tau = \frac{L}{R_{eq}}$$

$$R_{eq} = G + (20 \parallel 5) = G + \frac{20 \times 5}{20 + 5}$$

$$R_{eq} = 10 \Omega$$

$$\tau = \frac{0.5}{10} = 0.05 \text{ sec}$$

$$\therefore i_L(t) = 1.6 + (2 - 1.6) e^{-t/0.05} \text{ A}$$

$$i_L(t) = (1.6 + 0.4 e^{-20t}) \text{ A}$$

$$\therefore V_L(t) = L \frac{di_L(t)}{dt}$$

$$= 0.5 \frac{d}{dt} (1.6 + 0.4 e^{-20t})$$

$$\boxed{V_L(t) = -4 e^{-20t} \text{ V}} \quad t > 0$$

Likes: 3

Dislikes: 0
