

ID:

Name:

Brac University

Semester: Summer 2023

Course Code: CSE250

Circuits And Electronics

Section: 23


Faculty: PRM

Assessment: *Assignment-3*

- ✓ Submit softcopy online by deadline
- ✓ Submit hardcopy in class by deadline


■ Question 1 of 4 [CO2] [10 marks]

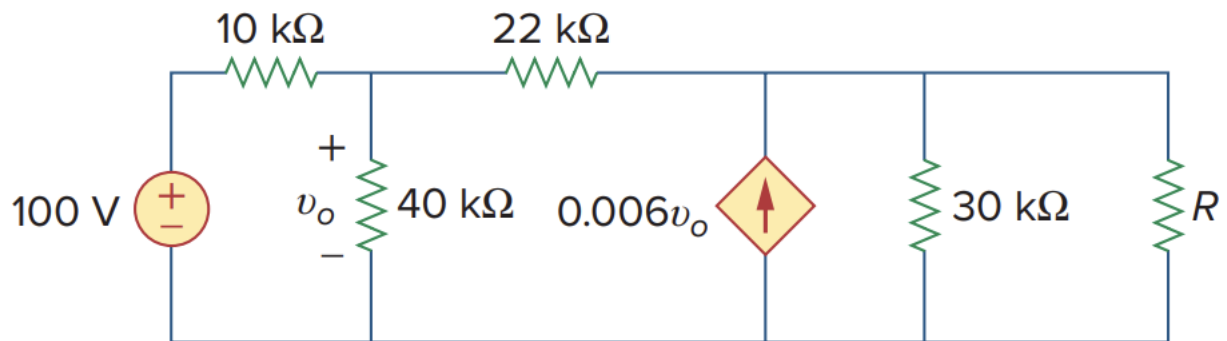Find the value of R which will give you the maximum output power. Also **find** the value of the maximum power.




■ Question 2 of 4 *[CO3] [10 marks]*

The Thevenin equivalent at terminals a-b of the linear network given below is to be determined. When a $10\text{-k}\Omega$ resistor is connected to terminals a-b, the voltage V_{ab} is measured as 20 V. When a $30\text{-k}\Omega$ resistor is connected to the terminals, V_{ab} is measured as 40 V. **Calculate:** (a) the Thevenin equivalent at terminals a-b, (b) V_{ab} when a $20\text{-k}\Omega$ resistor is connected to terminals a-b.

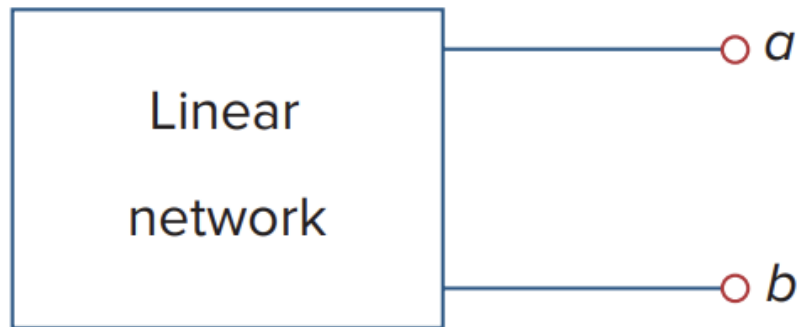

■ Question 3 of 4 *[CO3] [10 marks]*

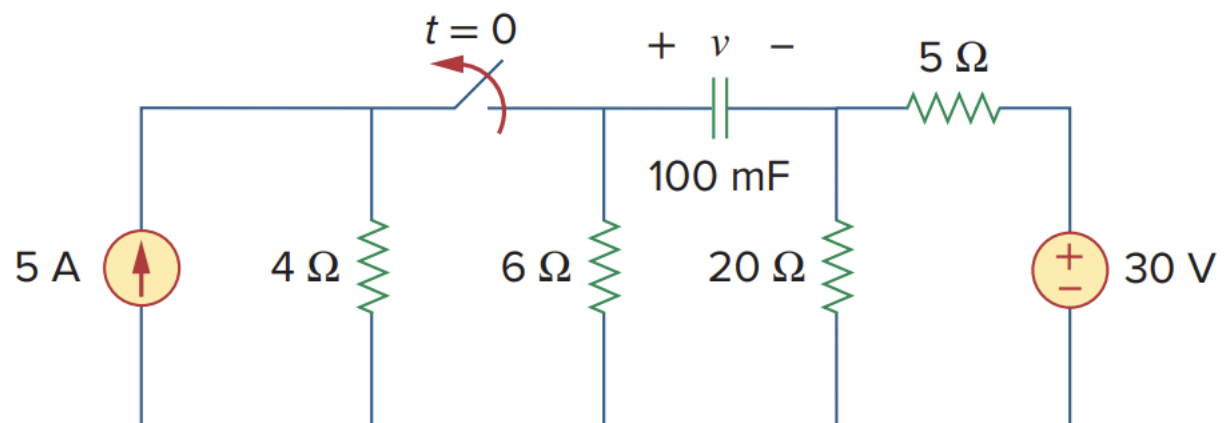Calculate $v(t)$ for $t < 0$ and $t > 0$.



■ Question 4 of 4 *[CO2] [10 marks]*

If $v_s=10\text{V}$ for $t<0$ and $v_s=30\text{V}$ for $t>0$, then **find** the value of v_o .

