

<< Search more Solutions!

Found Errors in Solution? >> [Report here!](#)

Answer

ANSWER


→ Use Superposition to solve for V_n in the circuit as shown in below figure.

→ The circuit has two Independent sources. Assume that the output voltage is


$$V_n = V_1 + V_2$$

Here V_1 and V_2 are the voltage response due to 4A current source and 6A current source respectively.

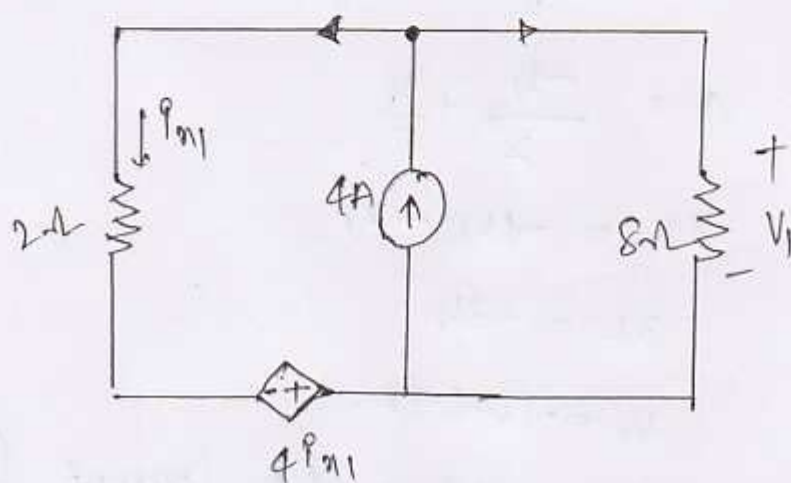To obtain V_1 set the 6A current source to zero as shown in following figure.



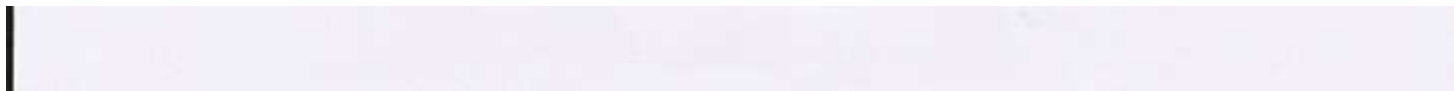Then, Applying Nodal Analysis at node V_1



$$4 = \frac{V_1 + 4I_{N1}}{2} + \frac{V_1}{8} \quad \text{--- (1)}$$

from circuit in figure (1) write the Krichhoff's Voltage Law around the outer loop.

$$V_1 = 2I_{N1} - 4I_{N1}$$

$$V_1 = -2I_{N1}$$

$$I_{N1} = -0.5V_1 \quad \text{--- (2)}$$

Substitute $-0.5V_1$ for I_{N1} in equation (1).

then we get,

$$4 = \frac{V_1 + 4(-0.5V_1)}{2} + \frac{V_1}{8}$$

$$4 = \frac{V_1 - 2V_1}{2} + \frac{V_1}{8}$$

$$4 = \frac{-V_1}{2} + \frac{V_1}{8}$$

$$32 = -4V_1 + V_1$$


$$32 = -3V_1$$

$$V_1 = -10.67V.$$

\therefore The O/p voltage when 4A Current Source Acting is $V_1 = -10.67V$



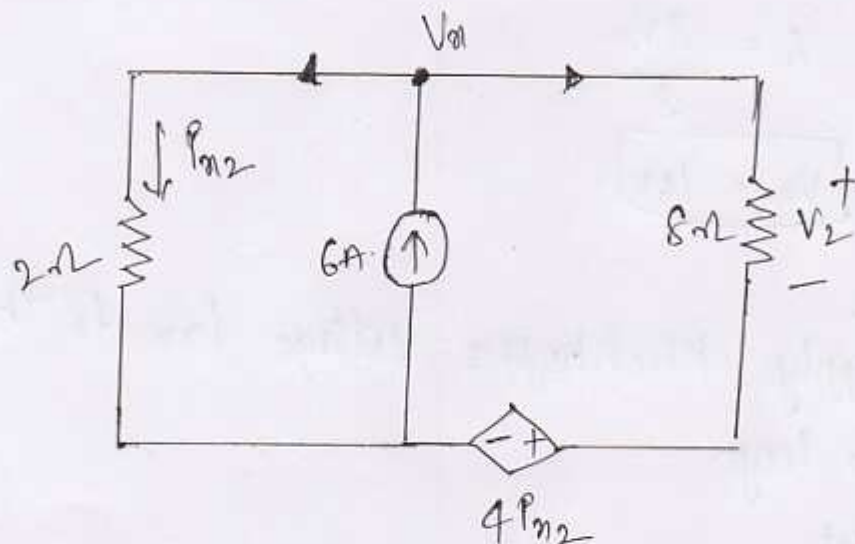→ Then
 To obtain V_2 , Set the 4A current source to zero as shown in the following figure.
 Shown below.



Then
 → Applying nodal analysis at node V_n .
 we get,

$$6 = \frac{V_n}{2} + \frac{V_n - 4I_{n2}}{8} \dots \dots (3)$$

from Above figure the current I_{n2} is

$$I_{n2} = \frac{V_n}{2} \dots \dots (4)$$

then,

Substitute $\frac{V_n}{2}$ for I_{n2} equation (3)

$$6 = \frac{V_n}{2} + \frac{V_n - 4\left(\frac{V_n}{2}\right)}{8}$$



$$6 = \frac{V_n}{2} + \frac{V_n - 2V_n}{8}$$

$$6 = \frac{V_n}{2} - \frac{V_n}{8}$$

$$6 = \frac{3V_n}{8}$$

$$\boxed{V_n = 16V}$$

→ Then,
Apply Kirchhoff's Voltage law to the right
side loop.

We get,

$$-V_n + V_2 + 4I_{n2} = 0.$$

Substituting $\frac{V_n}{2}$ for I_{n2} - replace.

$$-V_n + V_2 + 4 \left(\frac{V_n}{2} \right) = 0.$$

$$-V_n + V_2 + 2V_n = 0$$

$$V_2 + V_n = 0$$

$$V_2 = -V_n$$

$$V_2 = -16V.$$

$$\boxed{\therefore V_n = 16V}$$

$$\boxed{V_2 = -16V}$$



→ The output voltage when 6A current source
Acting $V_2 = -16V$.

→ Then
Add both the Responses to get the Actual
Output voltage V_n when both source Active.

$$\begin{aligned} V_n &= V_1 + V_2 \\ &= -10.67 - 16 \\ &= -26.67V \end{aligned}$$

Therefore,

The voltage V_n in the circuit is

$$\boxed{-26.67V}$$



Likes: 0

Dislikes: 0

